



# Abstract

---

This experiment aims to study the application of the op amp circuits such as adding, Voltage follower, Comparator, and Comparator with Hysteresis (Schmitt Trigger). As well investigate these circuits properties, measure characteristics like voltage gain using an oscilloscope, a digital voltmeter (DVM), and a DC power source in the laboratory.

# Table of Contents

Abstract .....	I
Table of Figures .....	III
Table of tables:.....	IV
Theory .....	1
1.Adding application: .....	1
2.Voltage Follower Application:.....	2
3.Voltage Comparator Application .....	2
4. Comparator with Hysteresis (Schmitt Trigger).....	4
5. Electronic components: .....	6
5.1: Oscilloscope:.....	6
5.2: DVM Digital Volt Meter: .....	6
Procedure and Data analysis .....	7
1. Adding Application: .....	7
1.1: Calculating $V_0$ : .....	7
2. Voltage Follower Application.....	8
3. Comparator Application.....	9
3.1 When $V_{DC} = 0$ Volt. ....	9
3.2 When $V_{DC} = -1.5$ Volt. ....	9
3.3 When $V_{DC} = 1.5$ Volt. ....	10
4. Comparator with Hysteresis (Schmitt Trigger):.....	11
Conclusion .....	13
References.....	14
Appendix.....	15

# Table of Figures

---

FIGURE 1 ADDER OP-AMP .....	1
FIGURE 2 VOLTAGE FOLLOWER [3].....	2
FIGURE 3 OP-AMP COMPARATOR.....	3
FIGURE 4 OP-AMP COMPARATOR WITH REFERENCE .....	3
FIGURE 5 SCHMITT TRIGGER .....	4
FIGURE 6 TRANSFER CHARACTERISTIC OF SCHMITT TRIGGER .....	5
FIGURE 7 TRANSFER CHARACTERISTIC OF SCHMITT TRIGGER WITH A SINUSOIDAL INPUT.....	5
FIGURE 8 OSCILLOSCOPE.....	6
FIGURE 9 DIGITAL VOLT METER .....	6
FIGURE 10 ADDING APPLICATION CIRCUIT .....	7
FIGURE 11 VOLTAGE FOLLOWER APPLICATION CIRCUIT.....	8
FIGURE 12 COMPARATOR APPLICATION CIRCUIT .....	9
FIGURE 13 COMPARATOR CIRCUIT OUTPUT WHEN $V_{DC} = 0VOLT$ .....	9
FIGURE 14 COMPARATOR CIRCUIT OUTPUT WHEN $V_{DC} = -1.5VOLT$ .....	9
FIGURE 15 COMPARATOR CIRCUIT OUTPUT WHEN $V_{DC} = 1.5VOLT$ .....	10
FIGURE 16 COMPARATOR OP AMP [10] .....	10
FIGURE 17 DIFFERENTIATOR OP AMP [9] .....	10
FIGURE 18 SCHMITT TRIGGER CIRCUIT .....	11
FIGURE 19 SCHMITT TRIGGER CIRCUIT SIMULATION .....	11
FIGURE 20 SCHMITT TRIGGER CIRCUIT SIMULATION WITH MEASUREMENT .....	11
FIGURE 21 LAB PAPER 1 ADDER TABLE .....	15
FIGURE 22 LAB PAPER 2 FOLLOWER TABLE .....	16

---

# Table of tables:

---

TABLE 1 MEASURED DATA OF V1, V2, V0 .....7

TABLE 2 VOLTAGE FOLLOWER VOLTAGE OUTPUT .....8

# Theory

## 1.Adding application:

Op-amp can be utilized to sum the input voltage of two or more sources into a single output voltage. Figure 1 is a circuit chart delineating the application of an op-amp as adder or summing amplifier.

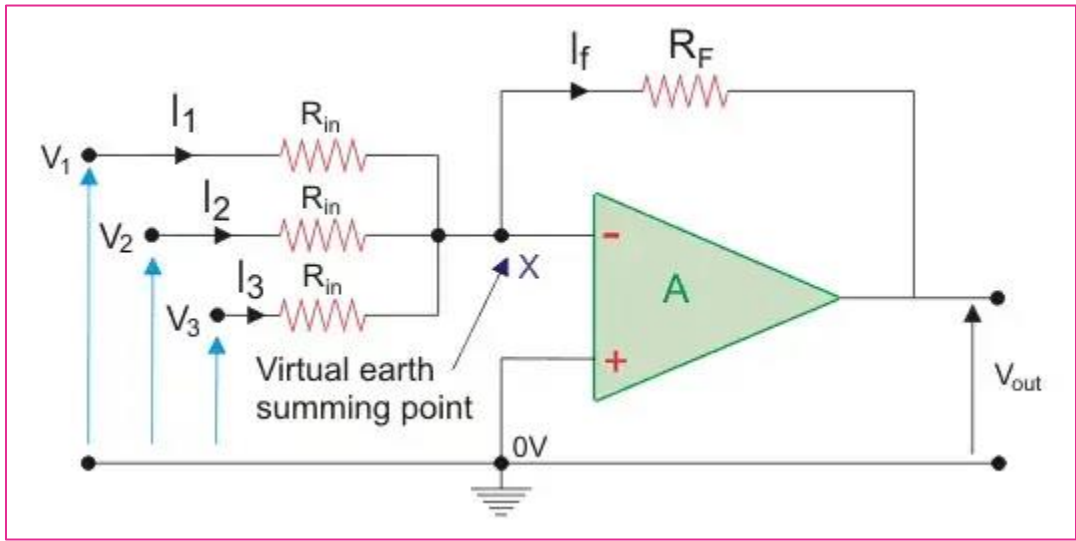


Figure 1 Adder op-amp

The input voltages are connected to the inverting terminal of the op-amp. The non-inverting terminal is connected to the ground. The output voltage is proportional to the entirety of the input voltages ( $V_{out}$ ) is the sum of the input voltages,  $V_1$ ,  $V_2$ ,  $V_3$ . [\[1\]](#) (7:45PM, 5/4/2024)

$$I_f = I_1 + I_2 + I_3 = - \left[ \left( \frac{V_1}{R_{in}} \right) + \left( \frac{V_2}{R_{in}} \right) + \left( \frac{V_3}{R_{in}} \right) \right]$$

$$\text{Inverting Equation: } V_{out} = - \frac{R_f}{R_{in}} \times V_{in}$$

$$\text{So } V_{out} = - \left[ \left( \frac{R_f}{R_{in}} \right) V_1 + \left( \frac{R_f}{R_{in}} \right) V_2 + \left( \frac{R_f}{R_{in}} \right) V_3 \right] \text{ in this case}$$

$$V_{out} = - \left[ \left( \frac{R_f}{R_{in}} \right) V_1 + \left( \frac{R_f}{R_{in}} \right) V_2 + \dots + \left( \frac{R_f}{R_{in}} \right) V_n \right] \text{ for } n \text{ input voltages.}$$

As the circuit can be modified to put more input voltages and follow the equation to get the desired output voltage.

## 2.Voltage Follower Application:

A voltage follower, also known as a noninverting buffer, other common names for the voltage follower are isolation amplifier, and unity-gain amplifier the output signal equal in amplitude to the input signal, Hence, the name of the follower that the output voltage directly follows the input voltage.

It operates with unity gain that is achieved through negative feedback. Without this feedback, the operational amplifier would display a high output voltage for any small input changes due to its high gain. [2]

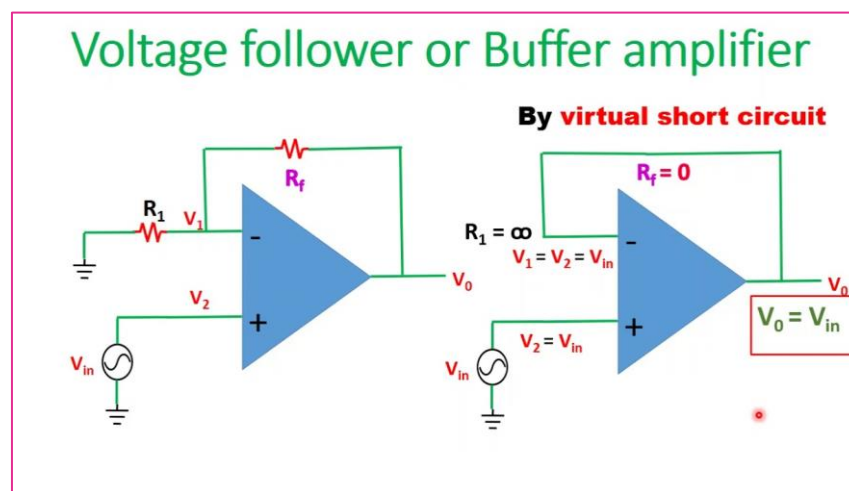


Figure 2 Voltage follower [3]

Since the op-amp is ideal, negative feedback ( $V_-$ ) reduces change by adjusting the output voltage ( $V_o$ ), to matches the voltage at the noninverting input terminal ( $V_+ = V_i$ ), So  $V_- = V_+ = V_i = V_o$ .

## 3.Voltage Comparator Application

The op-amp comparator compares two analog voltage levels or with a reference voltage and produces an output signal based on this comparison, specifying which input is larger. Unlike op-amps comparators operate with positive feedback or open-loop gain  $A_o$  so its output voltage is given by the expression:  $V_{OUT} = A_o (V_+ - V_-)$  where  $V_+$  and  $V_-$  correlate to the voltages at the non-inverting and the inverting terminals respectively.

This setup allows the comparator to switch between saturated states, either to its positive or negative supply(reference), due to its high open-loop gain. Meanwhile with reference when  $V_{IN}$  is less than the DC voltage level at  $V_{REF}$ , ( $V_{IN} < V_{REF}$ ), the output will be LOW and at the negative supply voltage,  $-V_{CC}$  resulting in a negative saturation of the output.

If the  $V_{IN}$  is increased above  $V_{REF}$ , the output rapidly switches to HIGH and reaches positive saturation. When the  $V_{IN}$  is slightly lower than  $V_{REF}$  again, the output switches back to negative saturation.

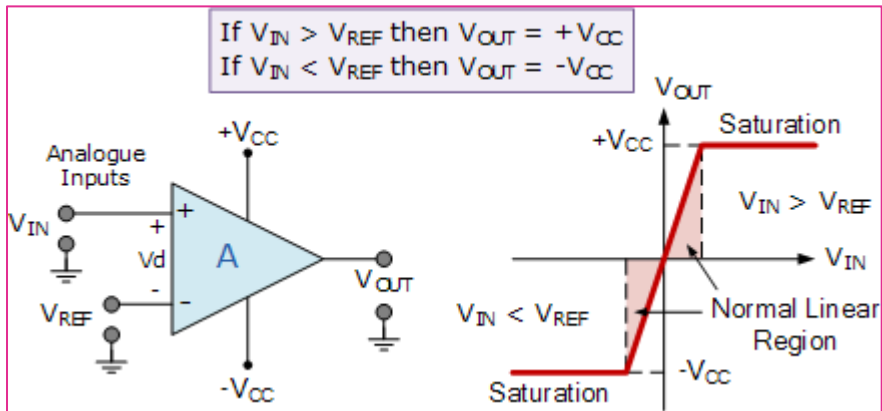


Figure 3 Op-Amp comparator

In theory the comparators reference voltage can be set to be anywhere between 0v and the supply voltage but there are practical limitations on the actual voltage range depending on the op-amp comparator being device used. [4]

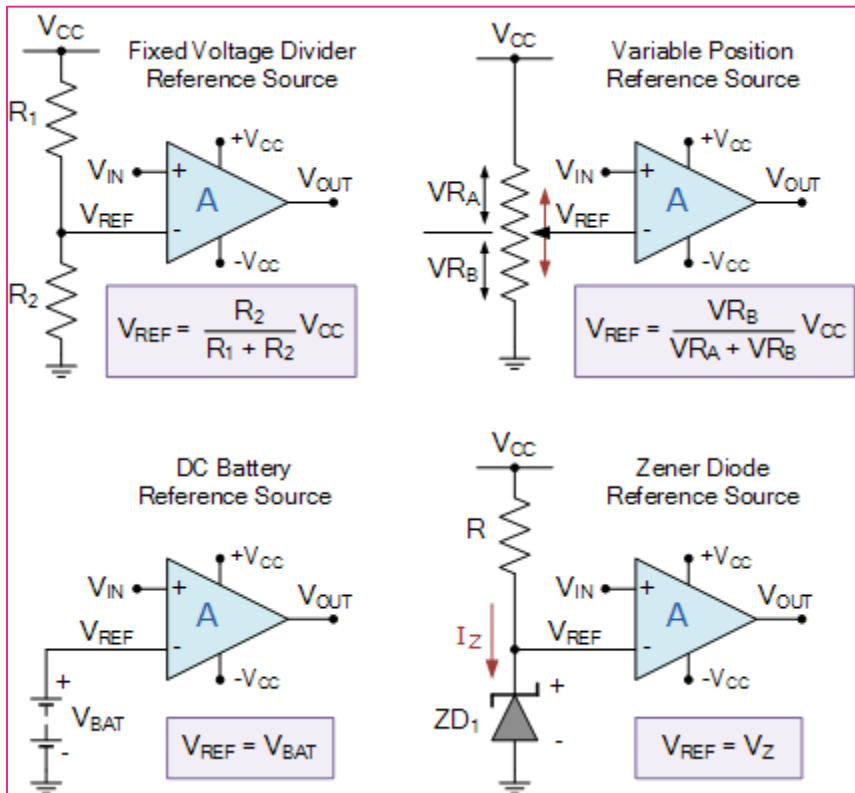


Figure 4 Op-Amp comparator with reference



## 4. Comparator with Hysteresis (Schmitt Trigger)

in an Inverting Schmitt Trigger, the input is applied to the inverting terminal of the Op-Amp. In this mode, the output produced is of opposite polarity. This output is applied to non-inverting terminal to ensure positive feedback.

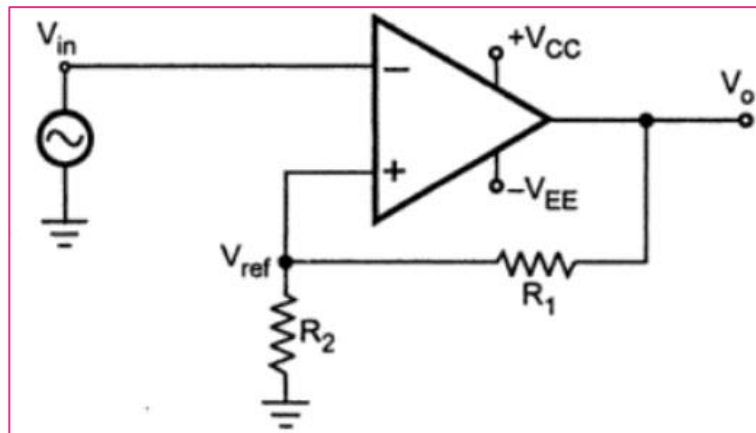


Figure 5 Schmitt Trigger

When  $V_{IN}$  is slightly greater than  $V_{REF}$ , the output becomes  $-V_{SAT}$  and if  $V_{IN}$  is slightly less than  $V_{REF}$  (more negative than  $-V_{REF}$ ), then output becomes  $V_{SAT}$ . Hence, the output voltage  $V_O$  is either at  $V_{SAT}$  or  $-V_{SAT}$  and the input voltage at which these state changes occur can be controlled using  $R_1$  and  $R_2$ .

The values of  $V_{REF}$  and  $-V_{REF}$  can be formulated as follows:

$$V_{REF} = \frac{(V_O \times R_2)}{(R_1 + R_2)}$$

But  $V_O = V_{SAT}$ . Hence,

$$V_{REF} = \frac{(V_{SAT} \times R_2)}{(R_1 + R_2)}$$

$$-V_{REF} = \frac{(V_O \times R_2)}{(R_1 + R_2)}$$

But  $V_O = -V_{SAT}$ . Hence,

$$-V_{REF} = \frac{(V_{SAT} \times R_2)}{(R_1 + R_2)}$$

The reference voltages  $V_{REF}$  and  $-V_{REF}$  are called Upper Threshold Voltage  $V_{UT}$  and Lower Threshold Voltage  $V_{LT}$ . The following image shows the output voltage versus input voltage graph. It is also known as the Transfer Characteristic of Schmitt Trigger.[\[5\]](#)

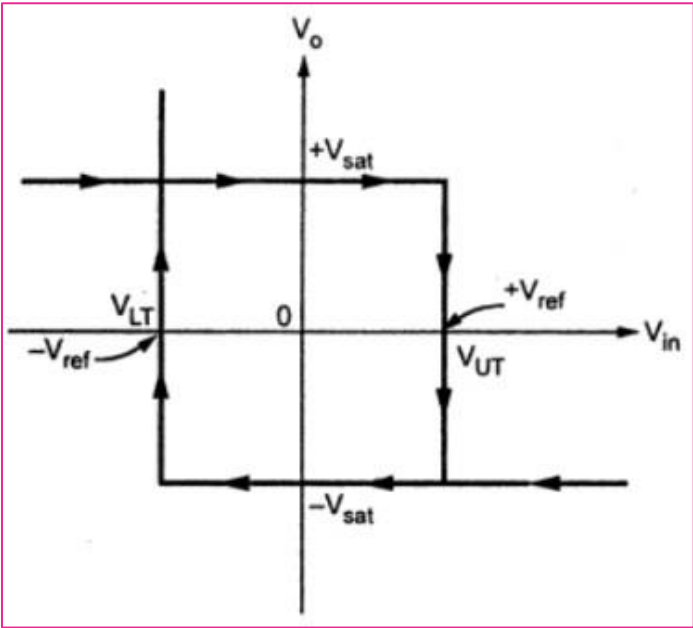


Figure 6 Transfer Characteristic of Schmitt Trigger

or as a pure sinusoidal input signal, the output of an Inverting Schmitt Trigger Circuit.

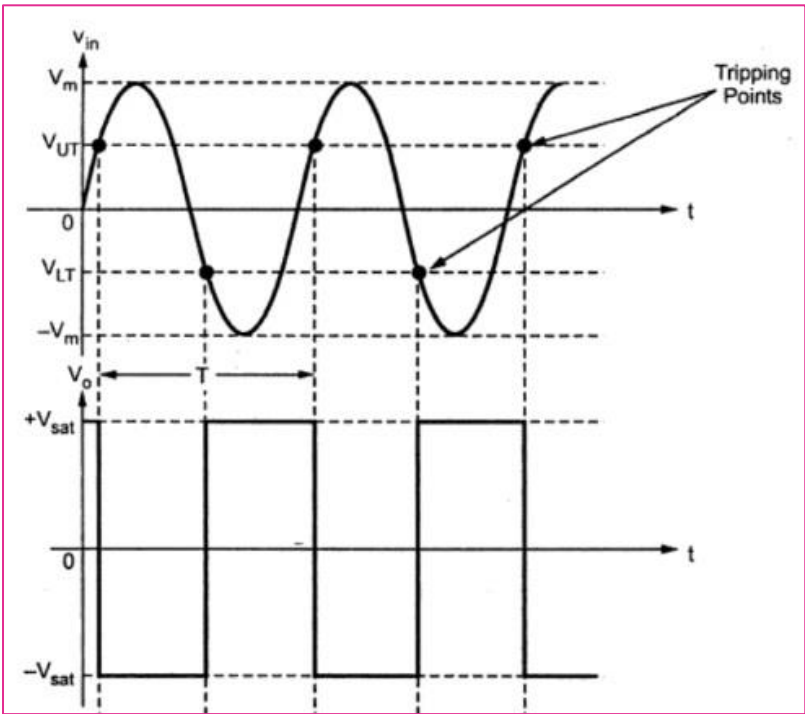


Figure 7 Transfer Characteristic of Schmitt Trigger with a sinusoidal input

5. Electronic components:

5.1: Oscilloscope:

Oscilloscope is the device used to measure time response in the circuits, it will display the output of the circuit as a graph of either voltage or current depending on the inputs connect to its channels.[\[11\]](#)

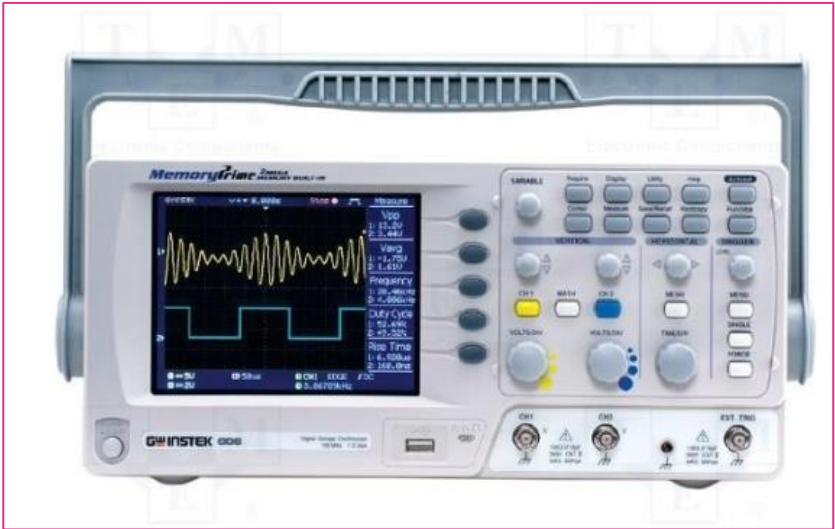


Figure 8 Oscilloscope

5.2: DVM Digital Volt Meter:

DMV is used to measure the voltage at which various appliances, the readings that a digital voltmeter offers are more accurate and fast as compared to analog meters. They are stable and hence, more reliable than earlier systems. They can measure both AC and DC voltage systems.[\[12\]](#)



Figure 9 Digital Volt Meter

# Procedure and Data analysis

## 1. Adding Application:

After the circuit in figure 10 has been connected, as V1 is controlled and adjusted by the potentiometer and V2 from DC source on trainer.

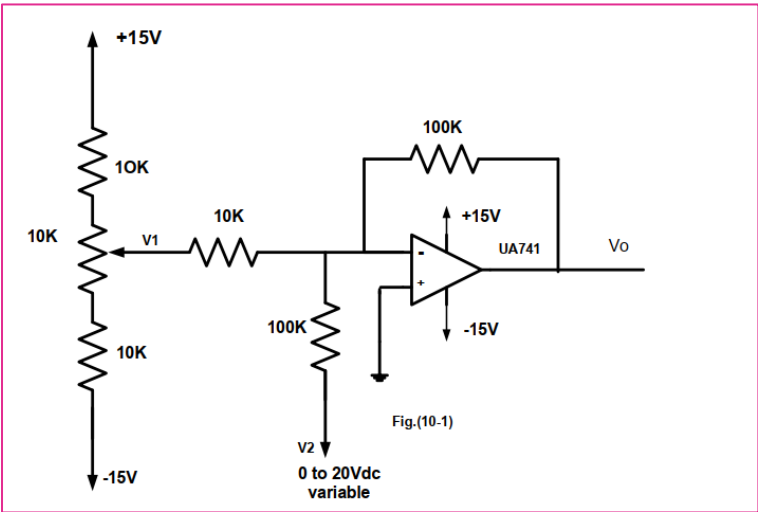


Figure 10 Adding Application circuit

V0 values has been measured as the following:

Table 1 Measured Data of V1, V2, V0

Input voltage		Output voltage	
V1	V2	V0	Calculated voltage
0.5	2	-7.147	-7
0.3	4	-7.028	-7
-0.9	2	7.002	7
-1.5	6	9	9

### 1.1: Calculating V0:

To calculate V0

$$V_o = - \left( \frac{R_F}{R_1} V_1 + \frac{R_F}{R_2} V_2 \right)$$
$$= - \left( \frac{100k}{10k} V_1 + \frac{100k}{100k} V_2 \right)$$
$$V_o = - (10 V_1 + V_2)$$

It has been n noticed how the values of V0 measured and calculated are almost identical with a small difference between them.

2. Voltage Follower Application

The circuit in figure 11 has been connected, and Vo has been connected to the oscilloscope.

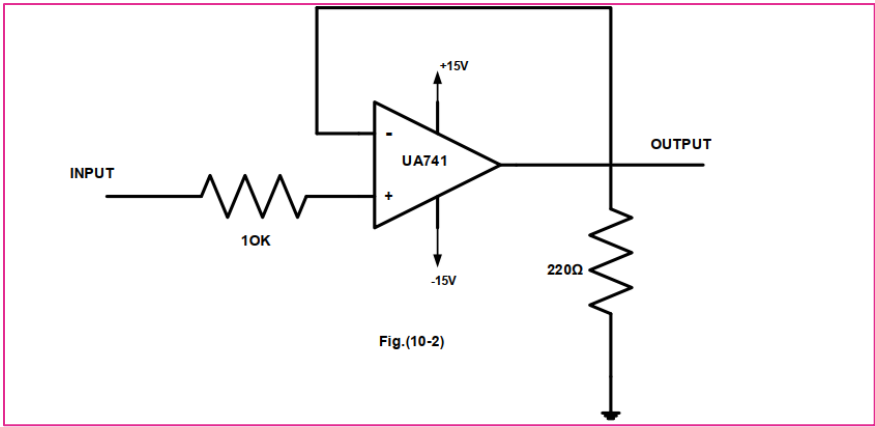


Figure 11 Voltage follower application circuit

Measurements of Vo for a dc input Vi by changing the connection from the DC trainer.

Table 2 Voltage Follower voltage output

Vi [DC, V]	1	3	4	5	6	7	8	10	12	14	15
Vo RL=220Ω	1.055	3.089	4.067	4.538	4.521	4.507	4.501	4.493	4.488	4.483	4.479
Vo RL=1kΩ	1.002	3.057	4.012	5	6.003	7.083	8.090	10.064	12.040	12.282	12.274

Questions Answers:

1. Both circuits provide isolation between the input and output signals. The emitter follower or common collector circuit provides an ideal buffer amplifier, and the op-amp acts as a voltage follower, producing an output voltage that closely tracks the input voltage. And both circuits have high input impedance and low output impedance.

2. Its used as a buffer in electronic logic circuits, isolation of input and output circuits, bridge circuits through a transducer, sample and hold circuits and in active filters. [6]

3.A. For 220Ohm:

Vo = Vi from 0 to around 4.5 until it reached the saturation mode  
Vo=Vmax = 4.538 for [4.5-15]

3.B. For 1kOhm:

Vo = Vi from 0 to around 12.2 until it reached the saturation mode  
Vo=Vmax = 12.282 for [12.2 -15]

An ideal op amp has no limits. Real ones do Because it’s not possible to drive an output beyond the power supply rails due to Kirchhoff Voltage Law (KVL). the sum of the voltages in any circuit loop must sum to zero and the power supply is algebraically “negative” and resistor, have positive voltage drops so the latter can never exceed the former.[7]

4.A. IMax = VMax / 220  
= 4.5380 / 220 = 20.6272mA

4.B. IMax = VMax / 1000  
= 12.282 / 1000 = 12.282mA

### 3. Comparator Application

The circuit in figure 12 has been connected, and  $V_o$  has been connected to the oscilloscope. DC reference has been changed in small steps from 0 to -1.5 and -1.5 As the following:


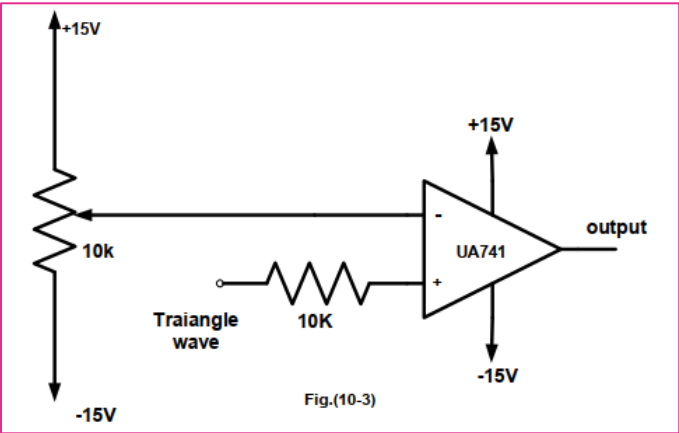


Figure 12 Comparator Application circuit

#### 3.1 When $V_{DC} = 0$ Volt.

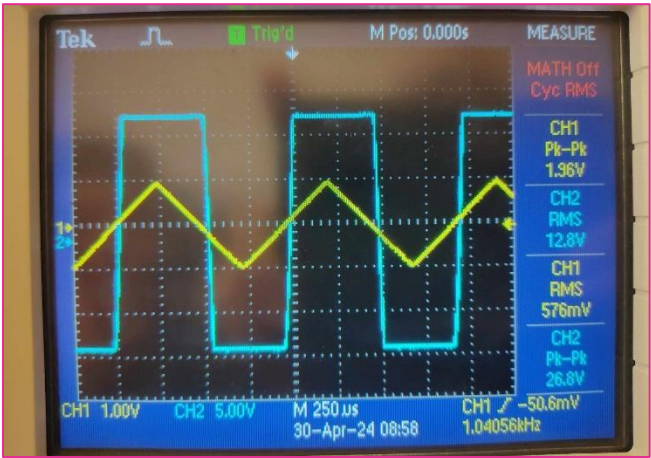

From figure 13: When  $V_{AC} > 0$  then  $V_{OUT} = V_{sat}$  and when  $V_{AC} < 0$  the output =  $-V_{sat}$ , as the input reference ( $V_{DC}$ ) is 0v, So the value of the output voltage is totally dependent on the supply voltage.

#### 3.2 When $V_{DC} = -1.5$ Volt.





From figure14:  $V_{OUT} = +V_{sat}$  as  $+V_{sat} = 200mV$  as the input ( $V_{DC}$ ) is  $-1.5v$ , as  $V_{AC} > V_{DC}$ .

3.3 When  $V_{DC} = 1.5\text{ Volt}$ .

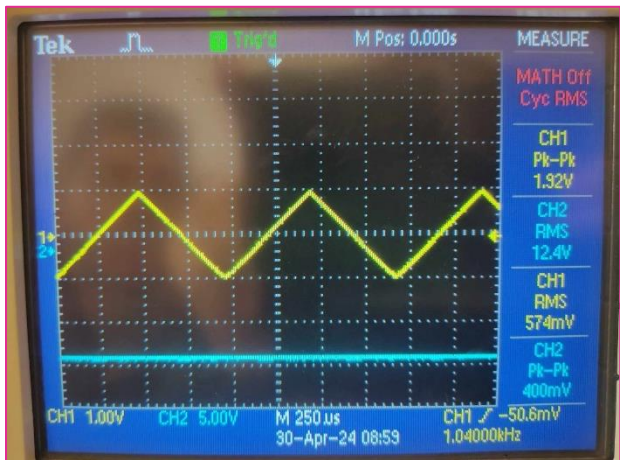


Figure 15 Comparator circuit output when  $V_{DC} = 1.5\text{Volt}$

From figure 15:  $V_{OUT} = -V_{sat}$  as  $-V_{sat} = 200mV$  as the input ( $V_{DC}$ ) is  $+1.5v$ , as  $V_{AC} < V_{DC}$ .

Questions Answers:

1.A. As has been seen through output pictures, when triangle input ( $V_{AC}$ )  $> 0$ ,  $V_{OUT}$  will equal to  $V_{sat}$  and when  $V_{AC}$  less than 0 the output =  $-V_{sat}$ , as the input reference ( $V_{DC}$ ) is 0v, So the value of the output voltage is only dependent on the supply voltage,  $V_{OUT}$  equal to zero when  $V_{AC} = V_{DC}$ .

The output shift to  $-V_{sat} = 200mV$  when the input reference ( $V_{DC}$ ) is  $+1.5v$  because  $V_{AC}$  is less than input reference.

The output shift to  $+V_{sat} = 200mV$  when the input reference ( $V_{DC}$ ) is  $-1.5v$  because  $V_{AC}$  is more than input reference.

1.B. Comparator used as Threshold detector, zero crossing detector, Schmitt trigger and Relaxation oscillator. [8]

2. The comparator can only provide  $+V_{sat}$  or  $-V_{sat}$ , whereas the diff amplifier can provide the difference of two voltages, therefore they do not share the same output, as example:

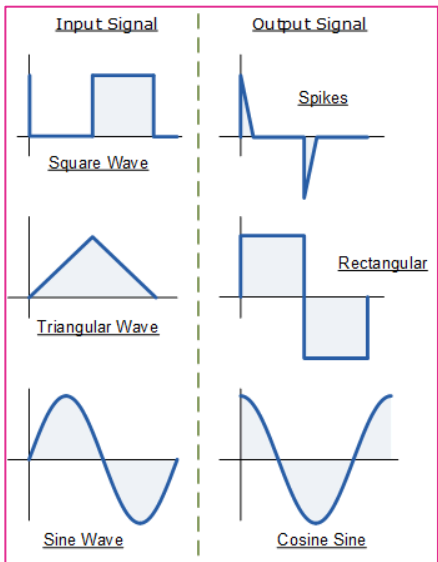


Figure 17 Differentiator op amp [9]

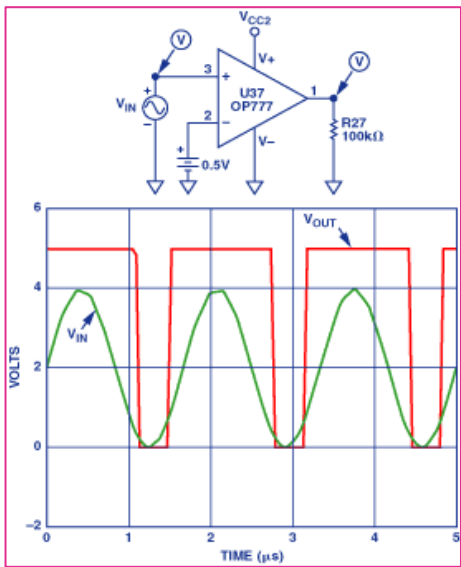


Figure 16 Comparator Op amp [10]

**4. Comparator with Hysteresis (Schmitt Trigger):**

The circuit in figure 18 has been connected,  $V_i$  is sat to be sinusoidal wave of frequency 1kHz and 15V<sub>P-P</sub>,  $V_o$  has been connected to the oscilloscope.


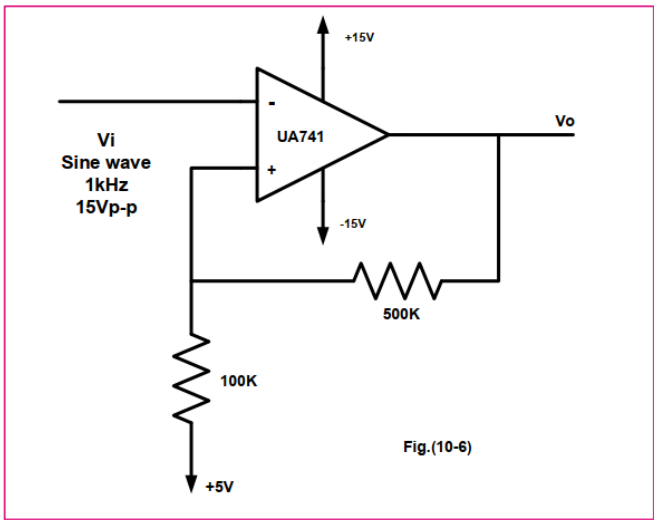


Figure 18 Schmitt trigger circuit

Which has given the following output:

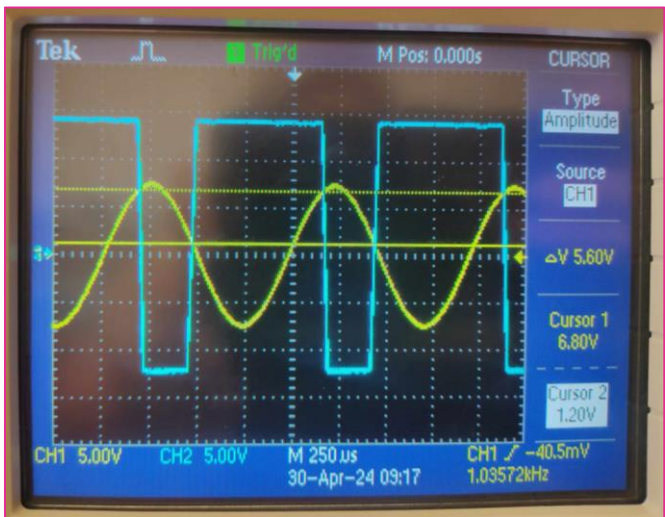

For measurement, the cursor has been used:





From figure 20,  $V_{UT}$  As Voltage of Upper threshold,  $V_{LT}$  As Voltage of Lower threshold

$$V_{UT} = 6.8 \text{ Volt.}$$

$$V_{LT} = 1.2 \text{ Volt}$$

Then the Hysteresis voltage can be given as:

$$\begin{aligned} V_H &= V_{UT} - V_{LT} \\ &= 6.8 - 1.2 \\ &= 5.6 \end{aligned}$$

$$\begin{aligned} V_{UT} &= \left( \frac{R_1}{R_1 + R_2} V_{sat} + \frac{R_2}{R_1 + R_2} (5) \right) \\ &= \left( \frac{100k}{600k} 13 + \frac{500k}{600k} 5 \right) \\ &= 6.333 \end{aligned}$$

$$\begin{aligned} V_{LT} &= - \left( \frac{R_1}{R_1 + R_2} V_{sat} \right) + \frac{R_2}{R_1 + R_2} (5) \\ &= - \left( \frac{100k}{600k} 13 \right) + \frac{500k}{600k} 5 \\ &= 2 \end{aligned}$$

Then the Hysteresis voltage can be given as:

$$\begin{aligned} V_H &= V_{UT} - V_{LT} \\ &= 6.3333 - 2 \\ &= 4.333 \end{aligned}$$

It has been noticed that the values are similar and close, yet there's a difference that's firstly due to  $V_{in}$  was close to 15, but it has been put to 15.2V, Leading the values to the Schmitt trigger to varies, as well as other errors in op-amp possibly or in the wires' impedance connection.

## Conclusion

---

In summary, the experiment shows the applications and the benefits of using feedback in electronic circuits. Through the use of different configurations such as inverting and noninverting adder amplifier, voltage follower, comparator and comparator with hysteresis (Schmitt trigger). The experiment also concluded that buffer feedback is a powerful circuit element that can be used to improve signal integrity, reduce noise and distortion, and provide stable gain in electronic systems

# References

---

- [1] <https://www.electrical4u.com/applications-of-op-amp/> [7:45 PM, 4 May 2024]
- [2] <https://www.allaboutcircuits.com/video-tutorials/op-amp-applications-voltage-follower/> [8:45 PM, 4 May 2024]
- [3] <https://www.youtube.com/watch?v=gtJPeh3HvHU> [9:30 PM, 4 May 2024]
- [4] <https://www.electronics-tutorials.ws/opamp/op-amp-comparator.html> [10 PM, 4 May 2024]
- [5] <https://www.electronicshub.org/schmitt-trigger-basics/> [11:10 PM, 4 May 2024]
- [6] <https://www.tutorialspoint.com/voltage-follower-using-operational-amplifier-definition-circuit-diagram-working-and-applications> [10:20 AM, 5 May 2024]
- [7] <https://www.quora.com/Why-does-the-output-of-the-op-amp-reach-a-limit-and-saturate-regardless-of-the-gain> [12:15 AM, 5 May 2024]
- [8] [https://en.wikipedia.org/wiki/Comparator\\_applications](https://en.wikipedia.org/wiki/Comparator_applications) [12:50 AM, 5 May 2024]
- [9] [https://www.electronics-tutorials.ws/opamp/opamp\\_7.html](https://www.electronics-tutorials.ws/opamp/opamp_7.html) [1:20 PM, 5 May 2024]
- [10] <https://www.analog.com/en/resources/analog-dialogue/articles/amplifiers-as-comparators.html> [1:20 PM, 5 May 2024]

# Appendix

## 1. Lab paper table of adder

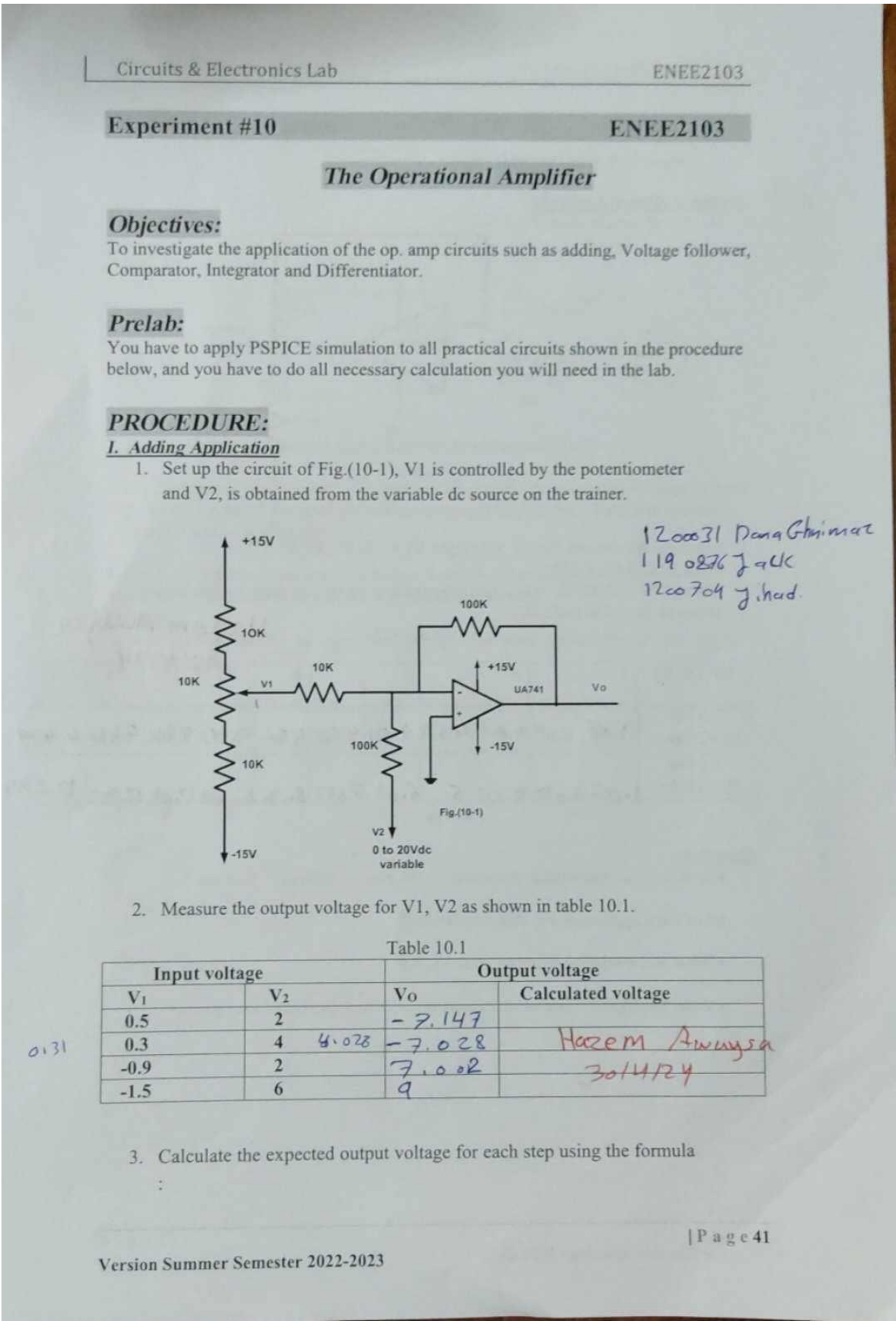


Figure 21 Lab paper 1 adder table

2. Lab paper follower table

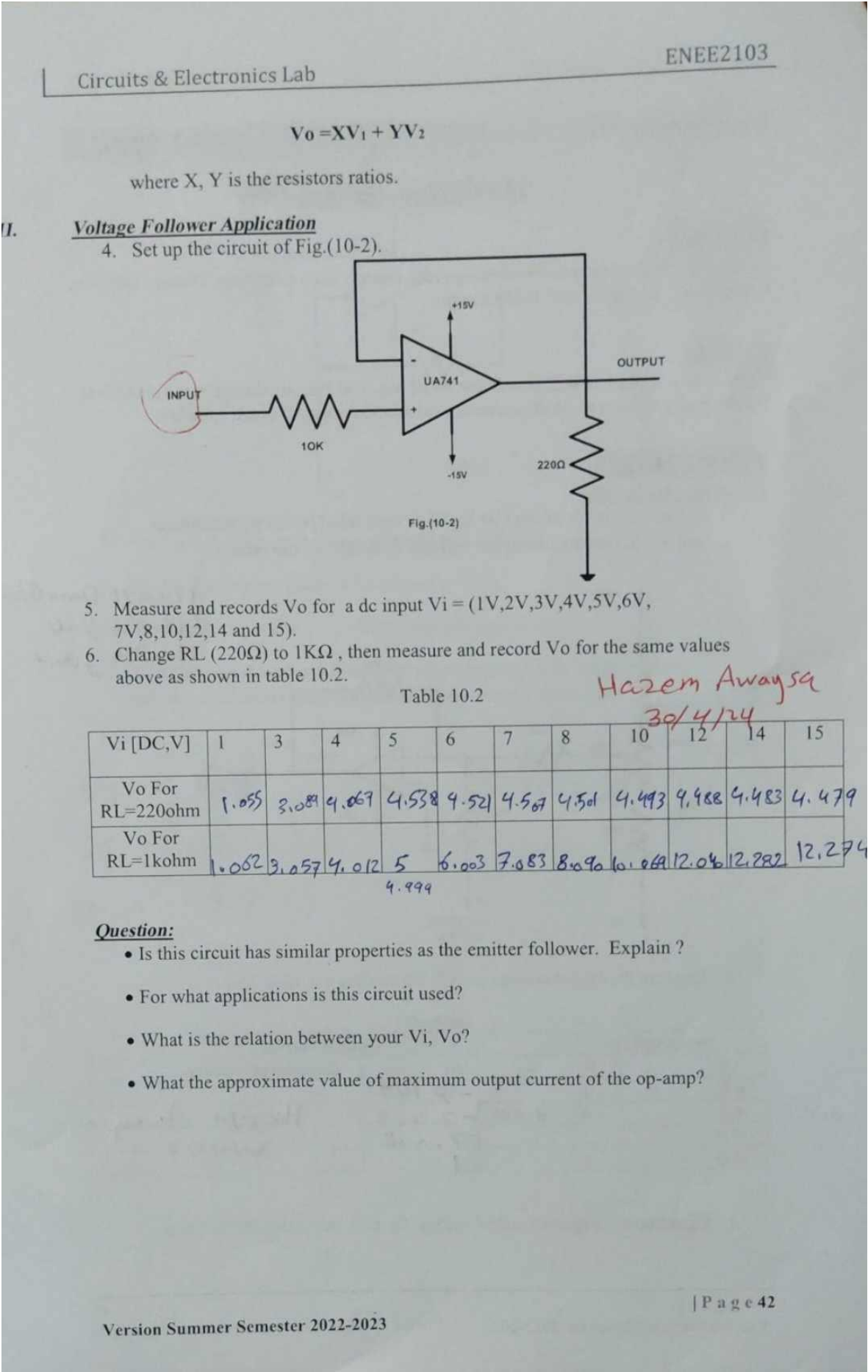


Figure 22 Lab paper 2 Follower table