



Faculty of Engineering and Technology
Electrical and Computer Engineering Department
CIRCUITS AND ELECTRONICS LABORATORY– ENEE2103
Experiment No. 10 Prelab
The Operational Amplifier

Prepared by:

Dana Ghnimat 1200031

Instructor:

Dr. Mohammad Jehad Al Ju'Beh

Assistant:

Eng. Hazem Awaysa

Section: 4

Date: 29/4/2024

Table of Contents

Table of Figures	II
Table of Tables	III
Prelab instructions:	1
Procedure and Discussion	2
Part 1: Adding Application	2
Part 2: Voltage Follower Application	4
Output Current when $R3 = 220\Omega$	4
Output Voltage when $R3 = 1k\Omega$:	5
Output Current when $R3 = 1k\Omega$	6
Part 3: Comparator Application	7
Part4: Comparator with Hysteresis (Schmitt Trigger)	10

Table of Figures

FIGURE 1 ADDING APPLICATION CIRCUIT	2
FIGURE 2 ADDING APPLICATION CIRCUIT SIMULATION	2
FIGURE 3 VOLTAGE FOLLOWER APPLICATION WHEN $R_L = 220\Omega$	4
FIGURE 4 INPUT AND OUTPUT VOLTAGE AND THE SATURATION MODE.....	4
FIGURE 5 INPUT CURRENT AND THE SATURATION MODE CURRENT	4
FIGURE 6 VOLTAGE FOLLOWER APPLICATION WHEN $R_L = 1K\Omega$	5
FIGURE 7 SATURATION MODE OUTPUT VOLTAGE	5
FIGURE 8 OUTPUT CURRENT AND SATURATION MODE	6
FIGURE 9 VOLTAGE COMPARATOR.....	7
FIGURE 10 VPULSE VALUES.....	7
FIGURE 11 V_O & V_{IN} & V_4 WHEN $V_3=0V$	7
FIGURE 12 V_O & V_{IN} & V_4 WHEN $V_3=-1.5V$	8
FIGURE 13 V_O & V_{IN} & V_4 WHEN $V_3=-1V$	8
FIGURE 14 V_O & V_{IN} & V_4 WHEN $V_3=1V$	8
FIGURE 15 V_O & V_{IN} & V_4 WHEN $V_3=1.5V$	9
FIGURE 16 COMPARATOR WITH HYSTERESIS (SCHMITT TRIGGER)	10
FIGURE 17 VSIN PARAMETERS.....	10
FIGURE 18 COMPARATOR WITH HYSTERESIS (SCHMITT TRIGGER) SIMULATION CALCULATED VALUES	10
FIGURE 19 COMPARATOR WITH HYSTERESIS (SCHMITT TRIGGER) SIMULATION	11

Table of Tables

TABLE 1 OUTPUT VOLTAGE.....3

Prelab instructions:

1. Simulate the circuits in the procedure section and determine the required values (set the parameters that must be assigned by the instructor in the procedure to proper values).
2. Verify if Simulation Results match the expected results

Procedure and Discussion

Part 1: Adding Application

the circuit has been sat up, V1 is controlled by the potentiometer and V2, is obtained from the variable dc source on the trainer.

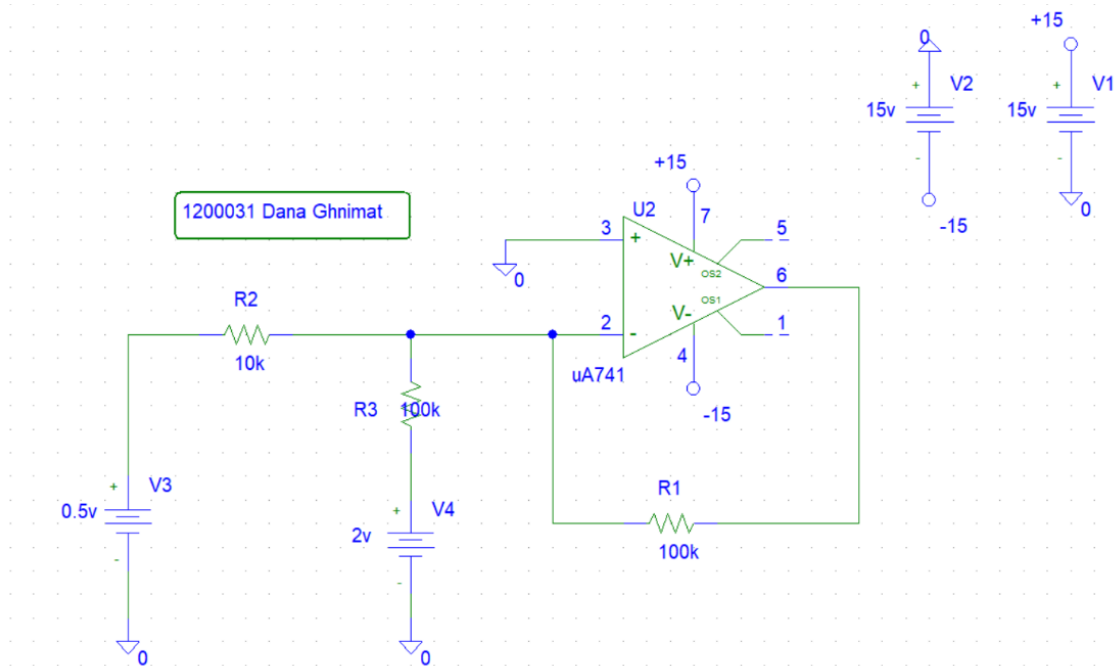


Figure 1 Adding Application Circuit

Simulation:

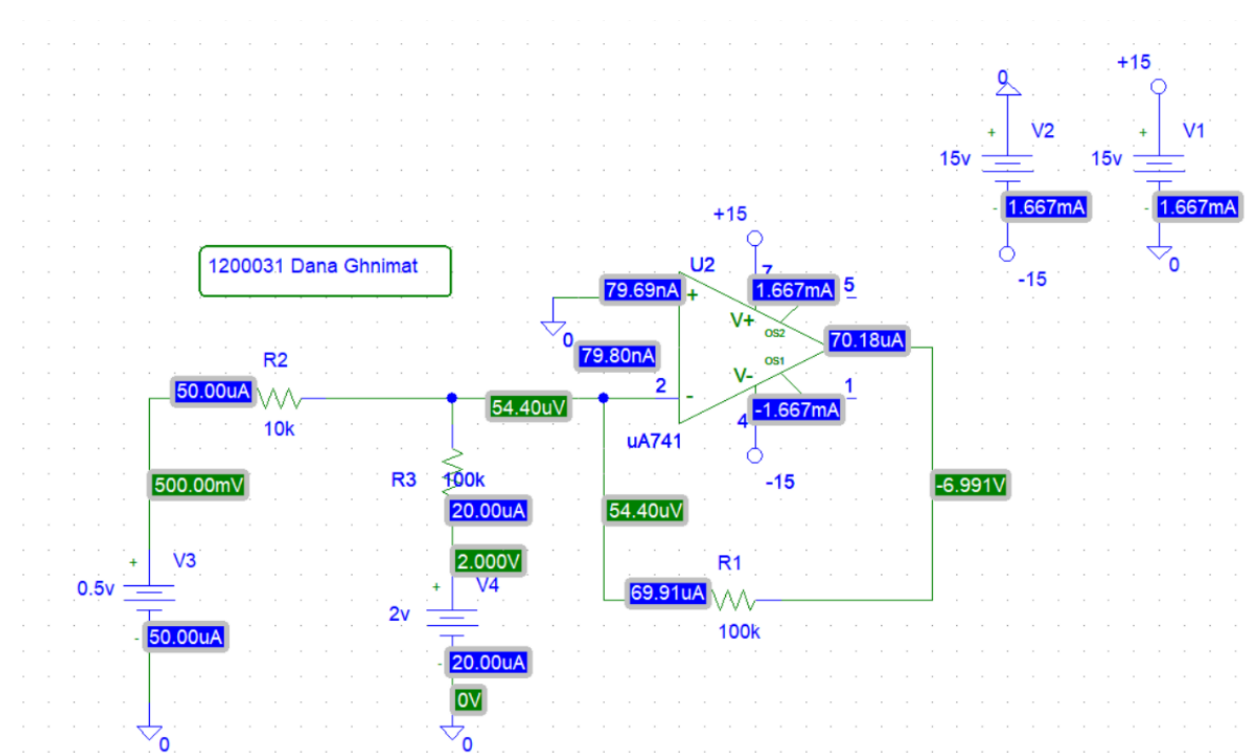


Figure 2 Adding Application Circuit Simulation

$$V_o = - \left(\frac{R_F}{R_1} V_1 + \frac{R_F}{R_2} V_2 \right)$$

$$= - \left(\frac{100k}{10k} V_1 + \frac{100k}{100k} V_2 \right)$$

$$V_o = - (10 V_1 + V_2)$$

Table 1 Output Voltage

Input Voltage		Output Voltage	
V ₁	V ₂	V _o	Calculated value
0.5	2	-6.991	− (10(0.5) + 2) = −7
0.3	4	-6.991	− (10(0.3) + 4) = −7
0.1	6	-6.991	− (10(0.1) + 6) = −7
-0.9	2	7.008	− (10(-0.9) + 2) = 7
-1.1	4	7.008	− (10(-1.1) + 4) = 7
-1.3	4	9.008	− (10(-1.3) + 4) = 9
-1.5	6	9.008	− (10(-1.5) + 4) = 9

Part 2: Voltage Follower Application

After the circuit has been sat:

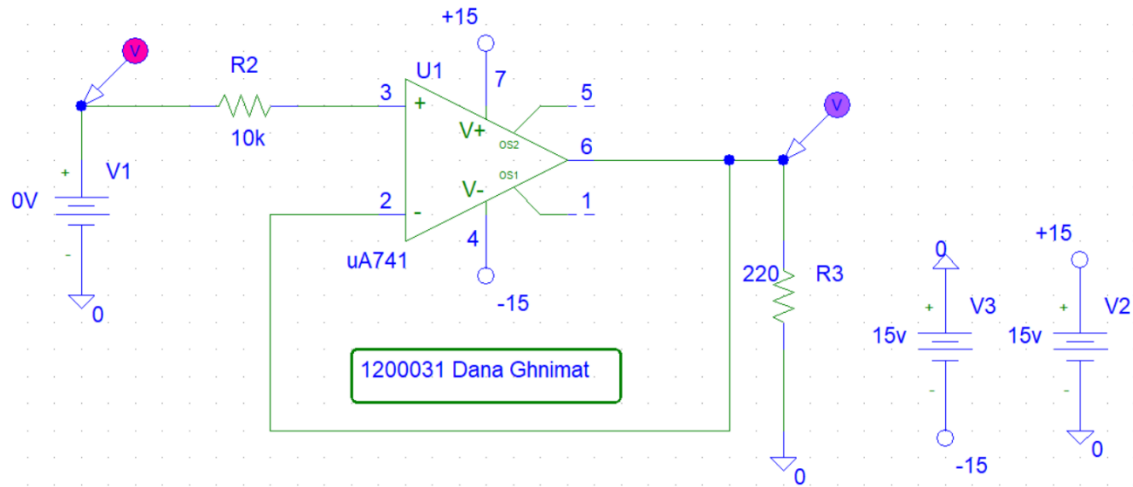


Figure 3 Voltage Follower Application when $R_L = 220\Omega$

To get the input and output voltage relation DC sweep has been used to records V_o for a dc input $V_i = (1 \text{ to } 20\text{V})$ using with a step of 1V.

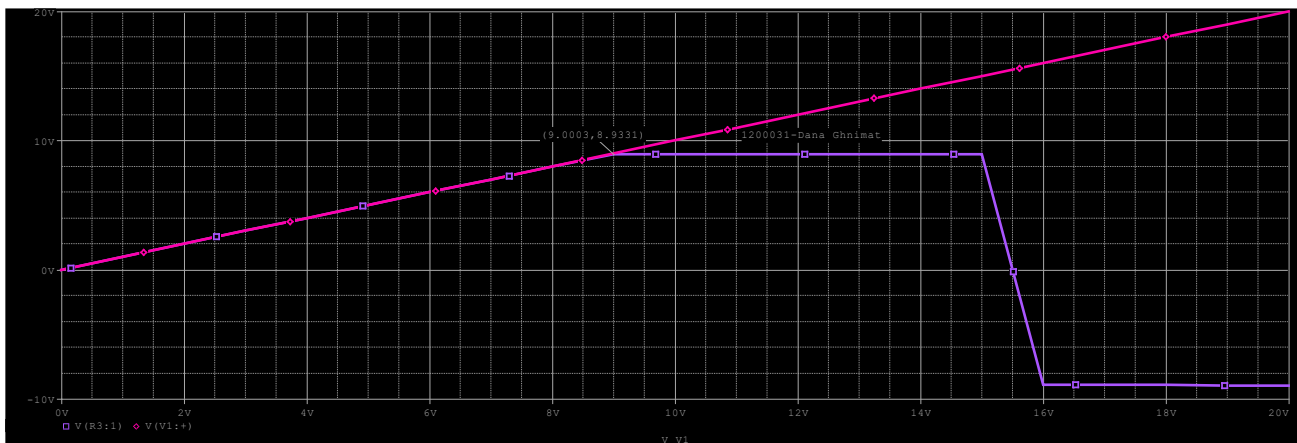


Figure 4 input and output voltage and the saturation mode

$V_o = V_i$ from 0 to around 9

$V_o = 8.9331$ for [9 -15]

$V_o = -8.9331$ for [15 -20]

Output Current when $R_3 = 220\Omega$:

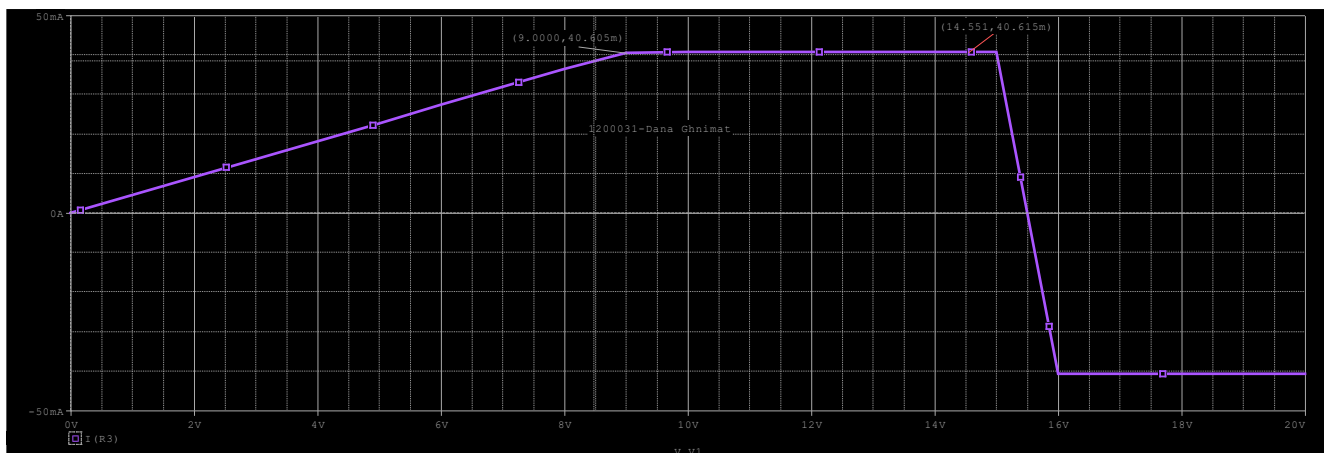


Figure 5 input Current and the saturation mode current

From Figure 5 from 0 to around 9, I_o is increasing linearly until it reaches 40.605mA, from 9 to 15, I_o at saturation mode which equals to 40.615mA.

I_o and V_o have the same characteristics. That means that Voltage follower and the current follower, which shows a unity gain maintaining a nearly one-to-one relationship between input and output voltages, as operational amplifier (op-amp) buffering voltage standard amp.

Output Voltage when $R_3 = 1k\Omega$:

After R_3 has been changed to $1k\Omega$.

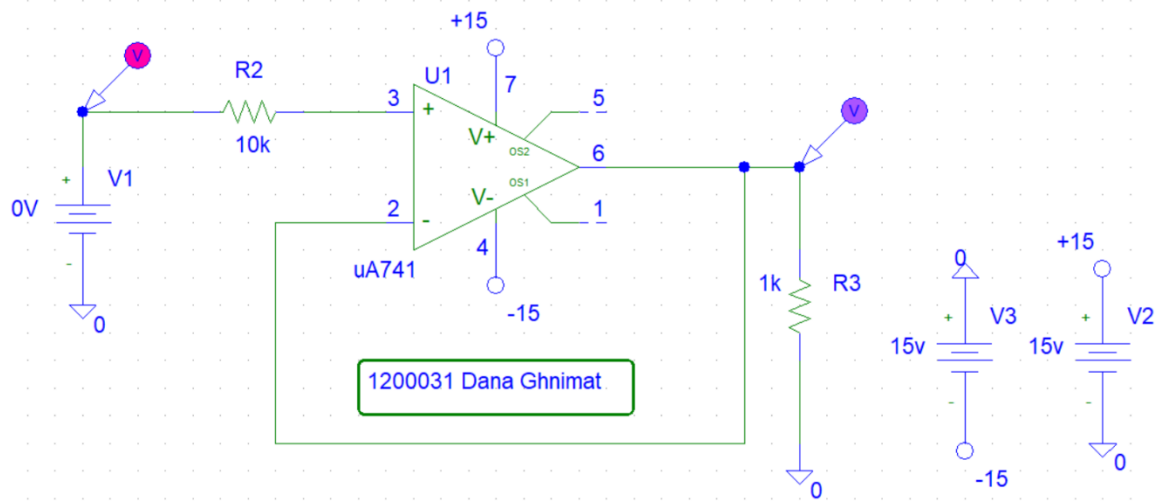


Figure 6 Voltage Follower Application when $R_L = 1k\Omega$

Simulation and saturation mode:

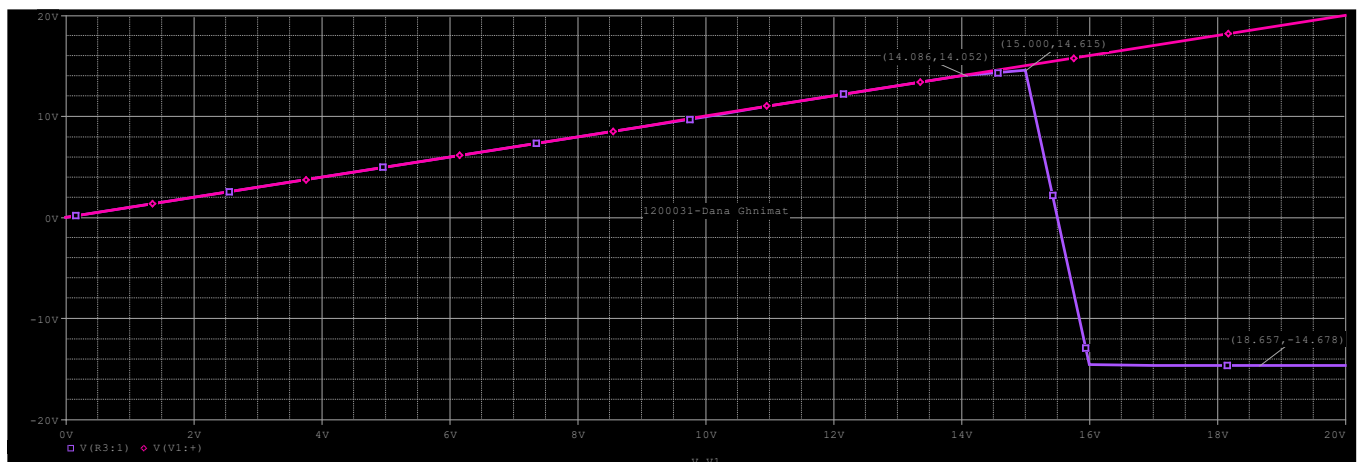


Figure 7 Saturation Mode Output Voltage

From Figure 7:

$V_o = V_i$ from 0 to around 14 (14.086)

$V_o = V_{max} = 14.615$ for [14.086-15]

$V_o = -14.678$ for [15 -20]

Output Current when $R_3 = 1k\Omega$

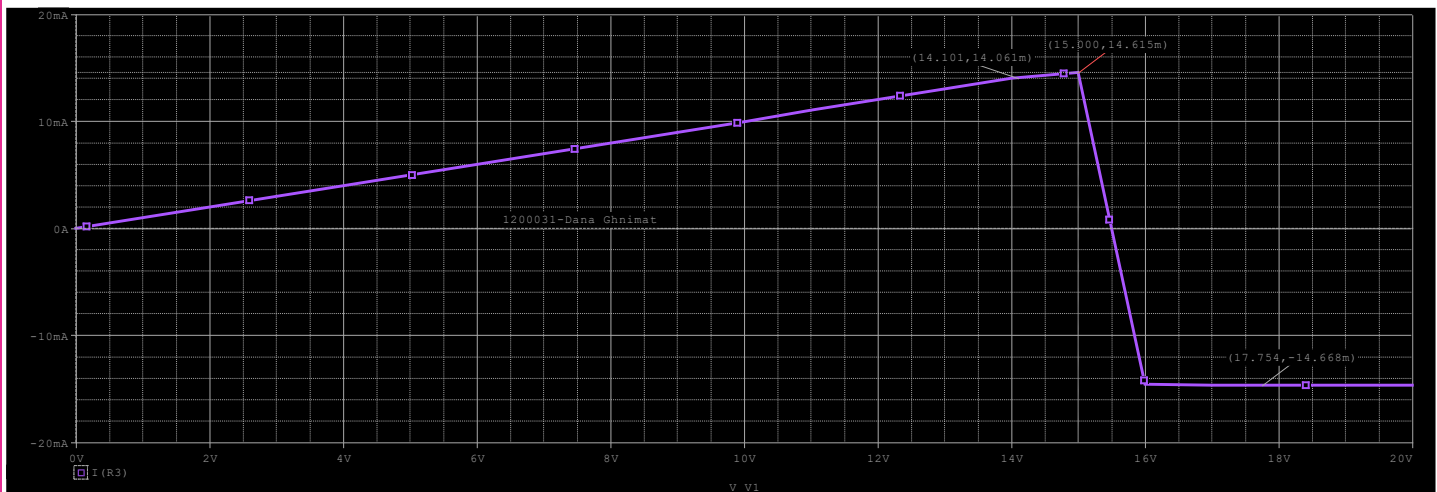


Figure 8 Output Current and Saturation Mode

From Figure 8 noted that from $[0 - \sim 14]$, I_o is increasing then stop from $]14 - 15]$, I_o at saturation mode equals 14.615mA.

I_o and V_o have the same characteristics. this indicates that Voltage follower and the current follower, shows a voltage gain close to unity, maintaining a nearly one-to-one relationship between input and output voltages.

Part 3: Comparator Application

The circuit of the comparator has been set up as the following:

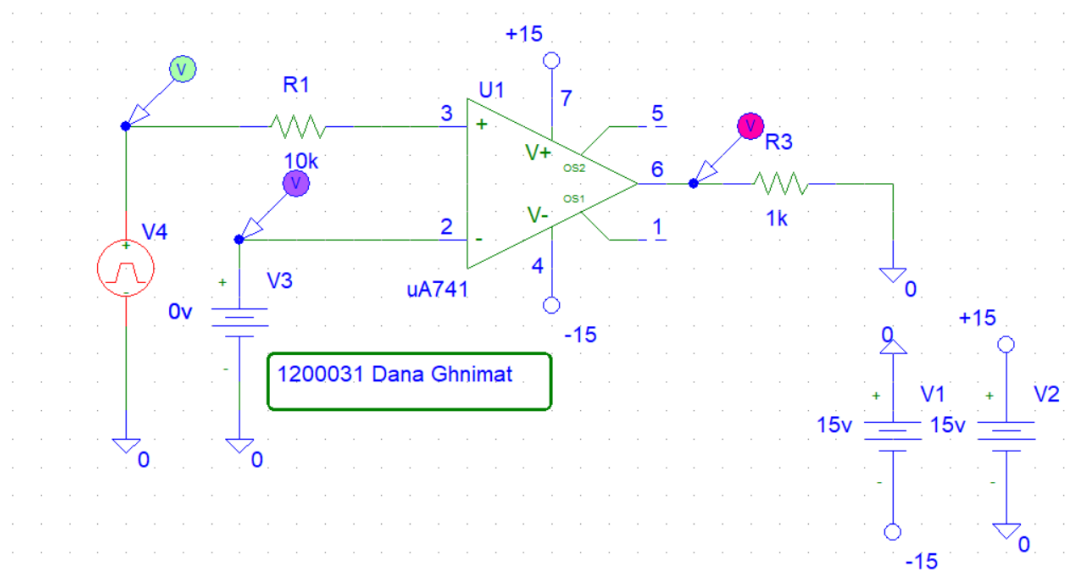


Figure 9 voltage comparator.

Vpulse values are: AC = 0, DC = 0,

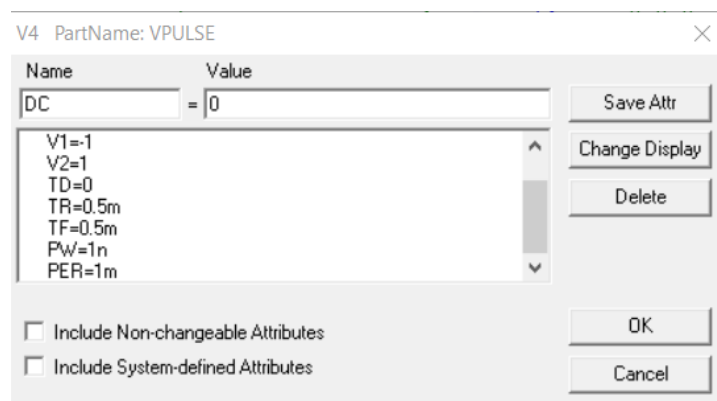


Figure 10 Vpulse values.

Simulation when V3 = 0V.

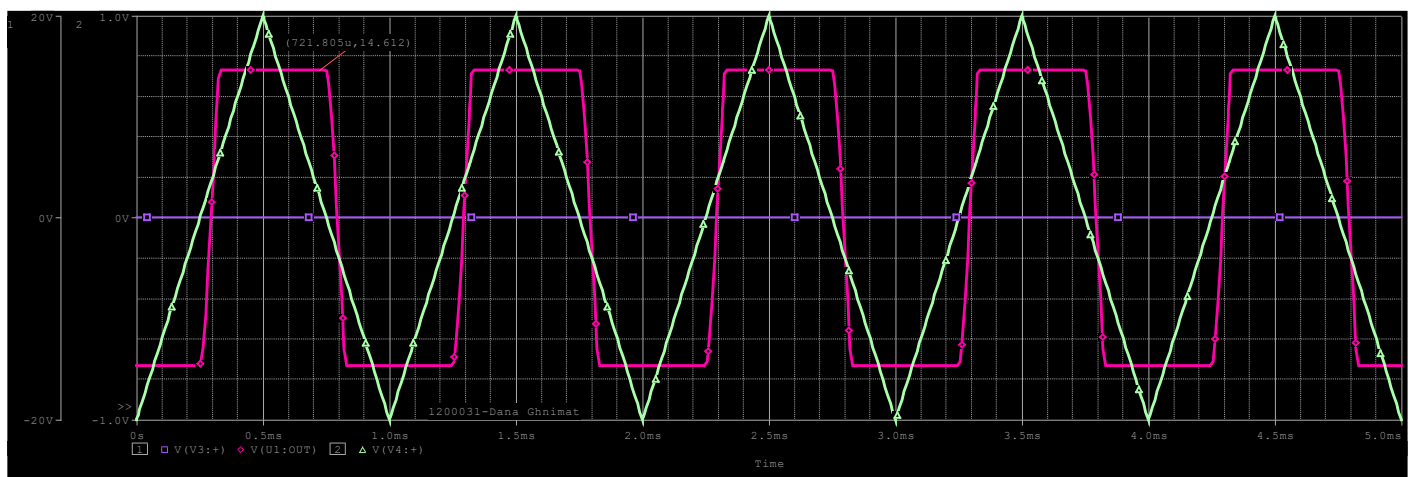


Figure 11 VO & Vin & V4 when V3=0V.

$V3 = -1.5V$

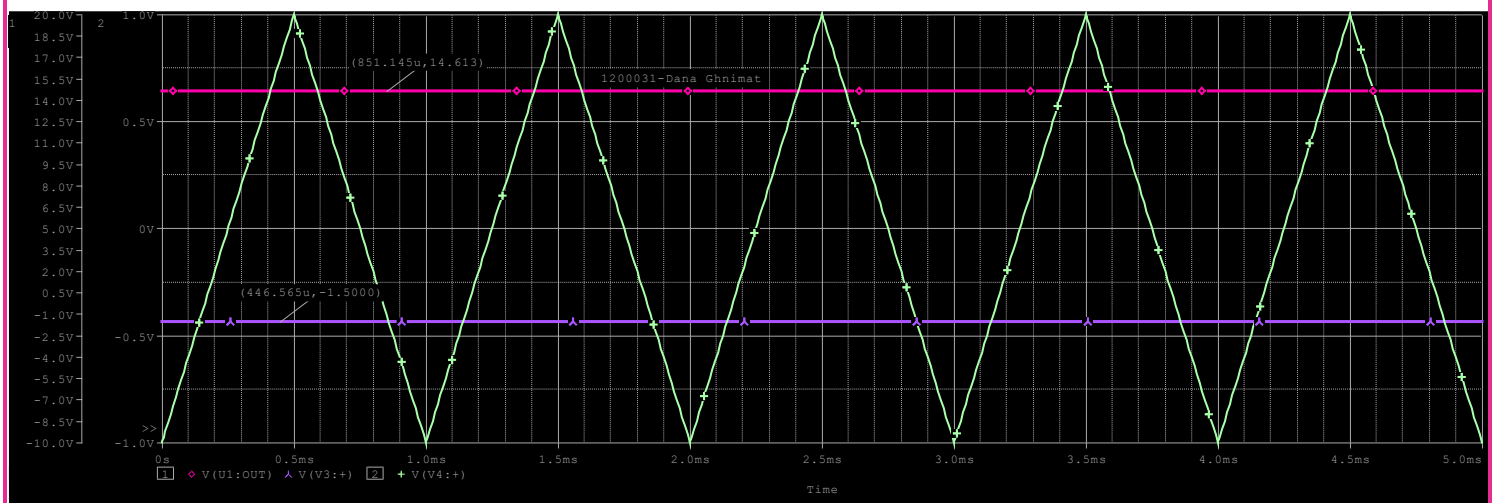


Figure 12 VO & Vin & V4 when $V3 = -1.5V$.

Figure 12 shows the input and output voltage as $-V_{sat}$ wave. with the potentiometer of 10k value and reverse the voltage on it.

$V3 = -1V$

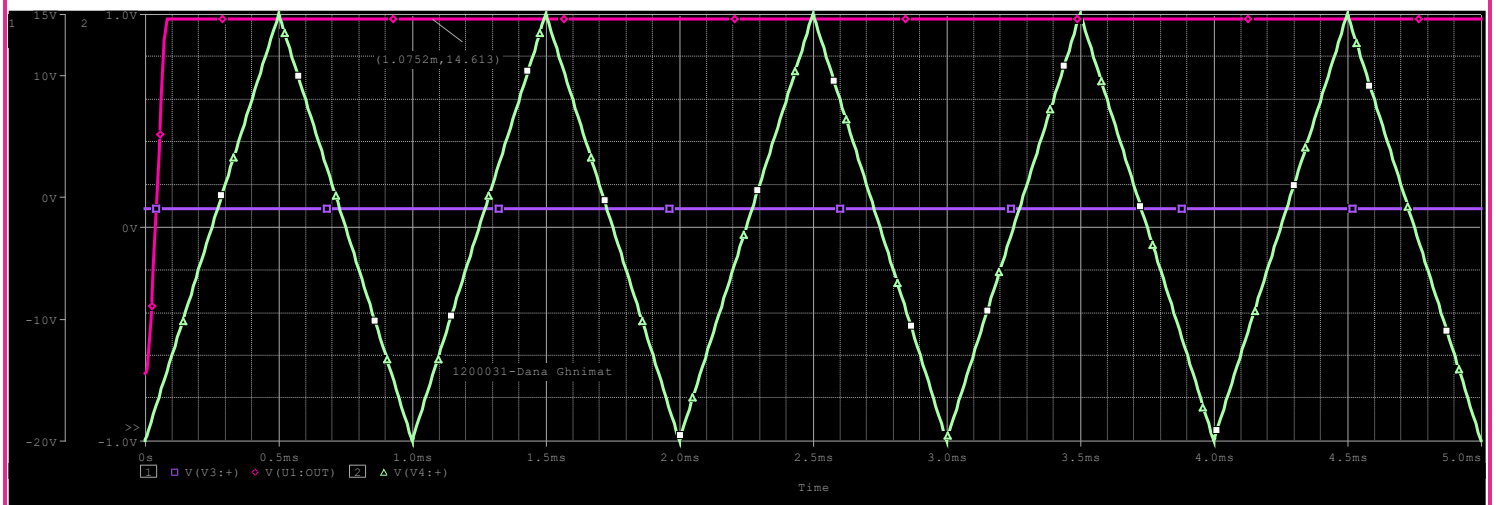


Figure 13 VO & Vin & V4 when $V3 = -1V$.

$V3 = 1V$

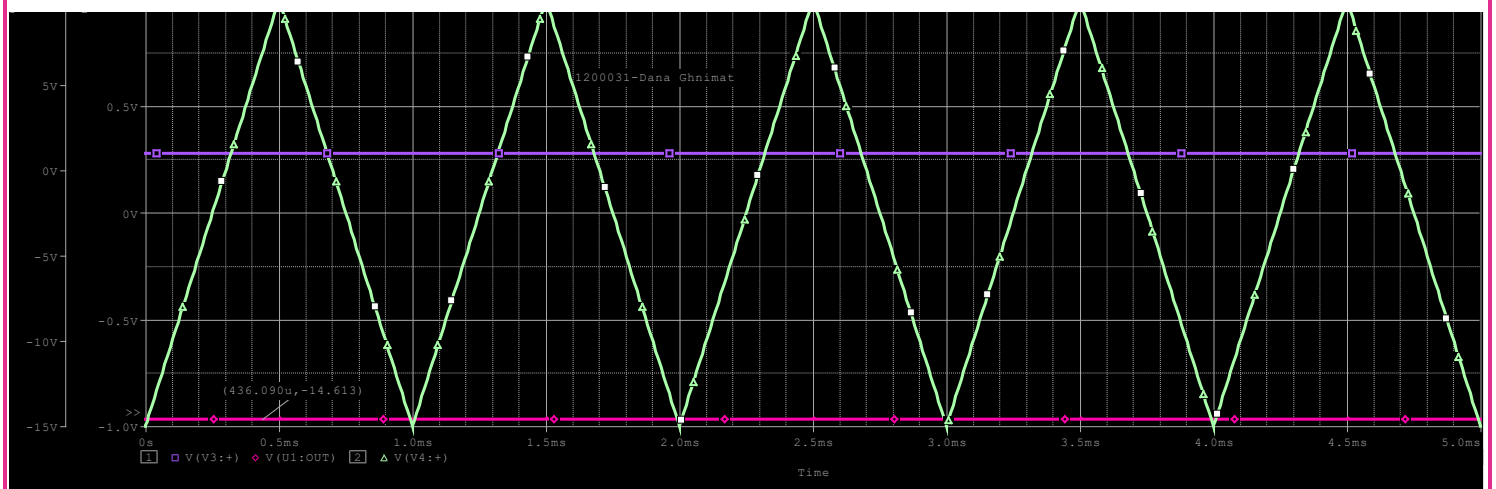


Figure 14 VO & Vin & V4 when $V3 = 1V$.

$V_3 = 1.5V$

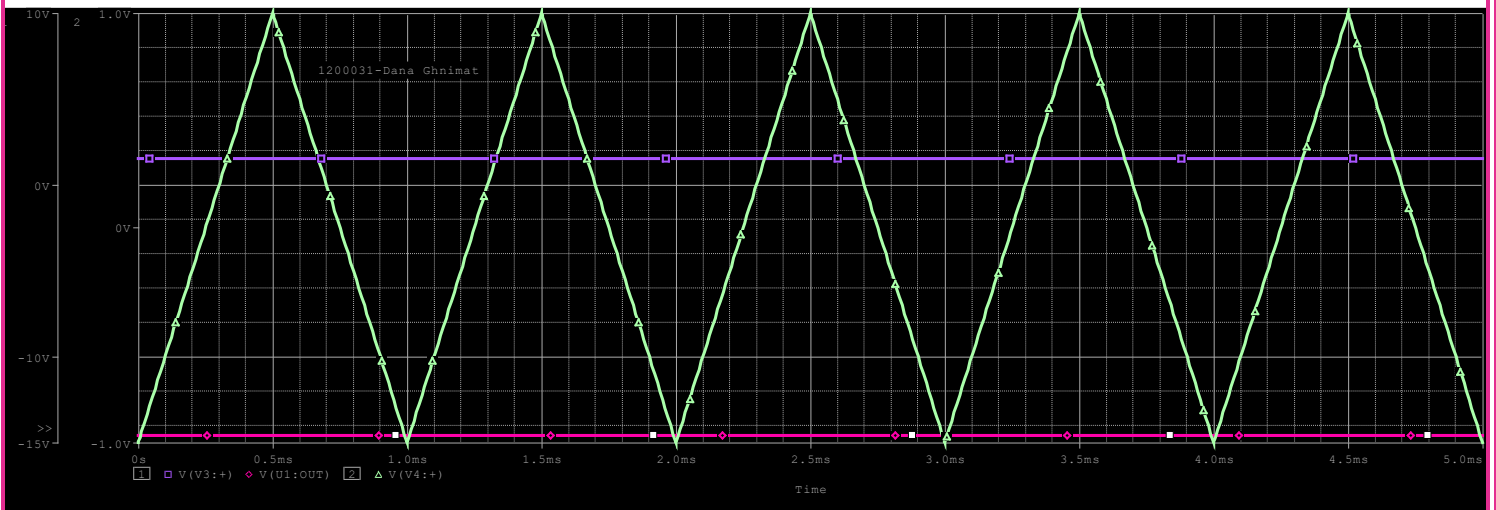


Figure 15 VO & Vin & V4 when $V_3=1.5V$.

Figure 15 shows the input and output voltage as $+V_{sat}$ wave.

Conclusion: In Opamp comparator

$$V(+)>V(-)\Rightarrow V_o=+V_{sat}$$

$$V(+)<V(-)\Rightarrow V_o=-V_{sat}$$

Part4: Comparator with Hysteresis (Schmitt Trigger)

Figure 16 shows comparator with Hysteresis circuit with input voltage have 15VPP and 1 kHz frequency

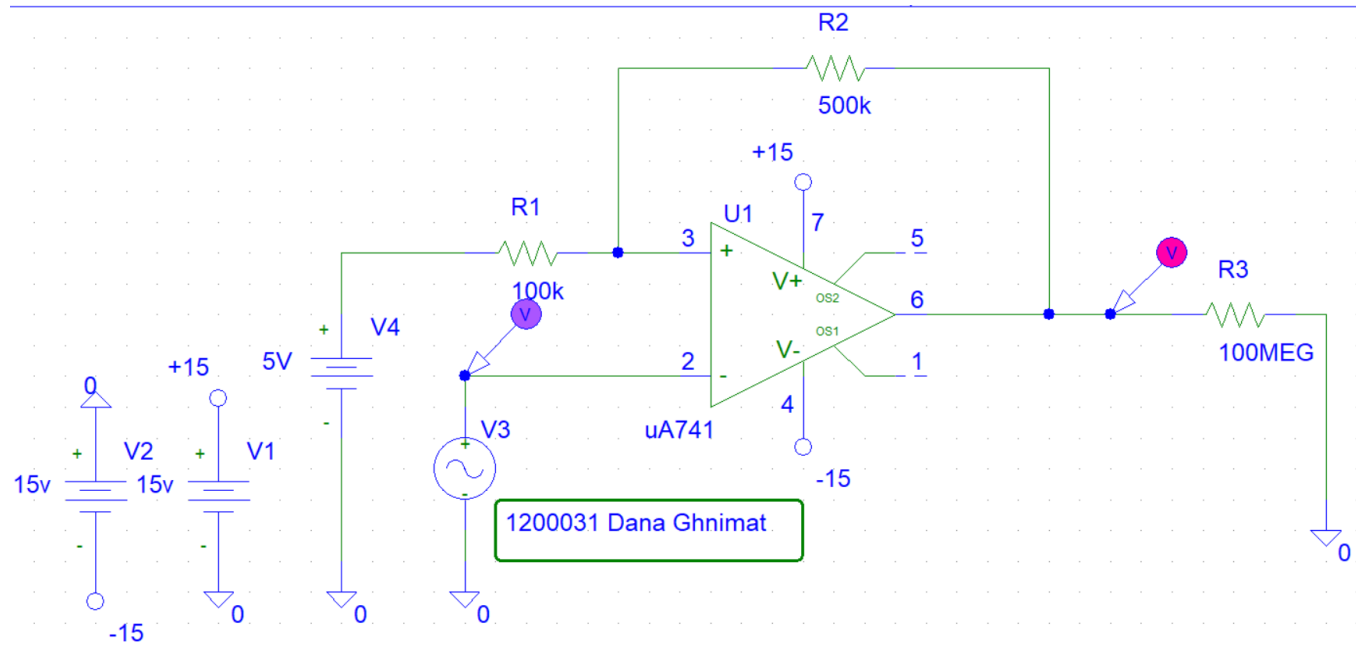


Figure 16 Comparator with Hysteresis (Schmitt Trigger)

Vsin parameters:

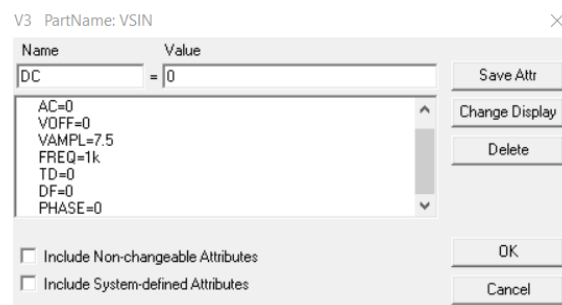


Figure 17 Vsin parameters

Simulation:

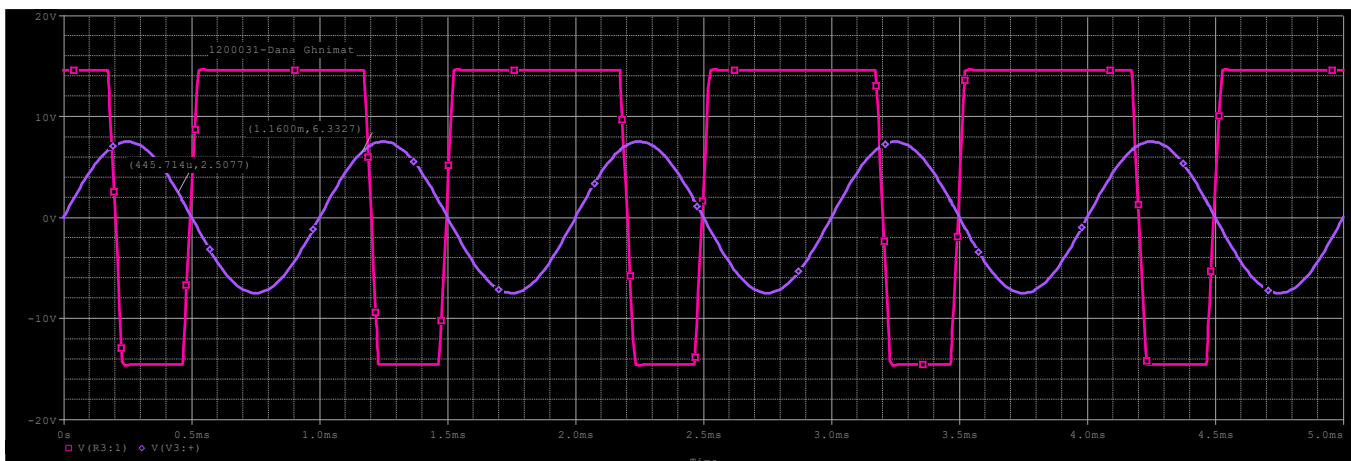


Figure 18 Comparator with Hysteresis (Schmitt Trigger) simulation calculated values

Simulation with practical values:

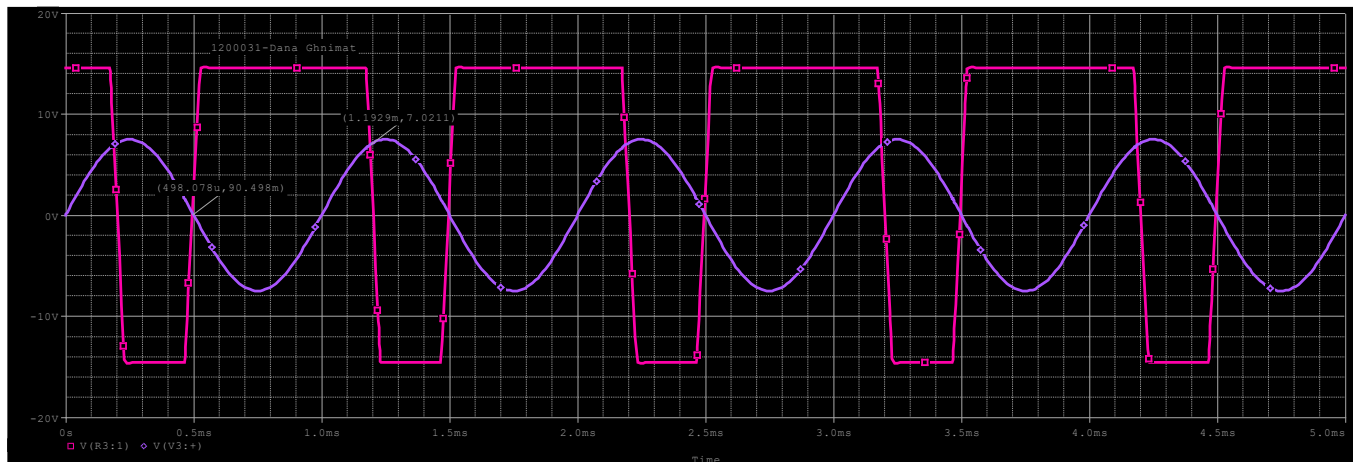


Figure 19 Comparator with Hysteresis (Schmitt Trigger) simulation

Practical values for $V_{UT} = 7.0211\text{V}$, $V_{LT} = 0.09076\text{mV}$

Mean while in calculations:

Note that $+V_{SAT} = V_{CC} - 2 = 15 - 2 = 13$

and $-V_{SAT} = -V_{CC} + 2 = -15 + 2 = -13$.

the upper threshold and lower threshold can calculate as:

$$V_{UT} = \left(\frac{R_1}{R_1 + R_2} V_{sat} + \frac{R_2}{R_1 + R_2} (5) \right)$$

$$\left(\frac{100k}{600k} 13 + \frac{500k}{600k} 5 \right)$$

$$= 6.333$$

$$V_{LT} = - \left(\frac{R_1}{R_1 + R_2} V_{sat} \right) + \frac{R_2}{R_1 + R_2} (5)$$

$$- \left(\frac{100k}{600k} 13 \right) + \frac{500k}{600k} 5$$

$$= 2$$

Then the Hysteresis voltage can be given as:

$$V_H = V_{UT} - V_{LT}$$

$$= 6.3333 - 2$$

$$= 4.333$$

When the voltage at one of a device's inputs changes, two additional voltage values are created to act as reference points.

The Lower Threshold Point is the lowest change point, while the Upper Threshold Point is higher change point.

Hysteresis voltage is the name for the subtraction between these two values.