



Faculty of Engineering and Technology

Electrical and Computer Engineering Department

CIRCUITS AND ELECTRONICS LABORATORY– ENEE2103

Experiment No. 7 Prelab

BJT Transistor as An Amplifier, CE, CC, CB Connection

Prepared by:

Dana Ghnimat 1200031

Instructor:

Dr. Mohammad Jehad Al Ju'Beh

Assistant:

Eng. Hazem Awaysa

Section: 4

Date: 1/4/2024

Table of Contents

Table of Figures	II
Table of Tables	III
Prelab instructions:	1
Procedure and Discussion	2
Part 1: Common emitter transistor amplifier	2
1.1: 0 Voltage Ac and Dc (CE amplifier with voltage divider - bias):	2
1.2: 8 Voltage DC value:	2
1.3: When voltage 1V AC:	3
1.4: 8 Voltage DC value and 2.2volt AC:	3
1.5: Gain calculation on Vb and Vo.....	4
1.6: The effect of the 100 k Ω Resistor	5
Part 2: Common collector transistor amplifier:	7
2.1: CC Transistor Amplifier Circuit	7
2.2: Vo is about 2 volts peak-to-peak.....	7
2.3: Calculating Ai and Zi:	8
2.4: Calculating Zout:	8
2.5: I _{in} for 100k Ω Register:	10
Part3: Common base transistor amplifier:	11
3.1: Common Base Transistor Circuit:	11
3.2: Setting V _{out, p-p} to 2V:	12
3.3: Calculating Zi and Ai:	12
3.4: V across 0.47k Ω Resistor:	13
3.5: I _{in} for 10k Ω resistor:	13
3.6: Calculating Zout:	14

Table of Figures

FIGURE 1 CE AMPLIFIER WITH 0 VOLT	2
FIGURE 2 CE AMPLIFIER WITH DC POWER SUPPLY	2
FIGURE 3 CE AMPLIFIER VOUT WHEN VI = 1V	3
FIGURE 4 CE AMPLIFIER VOUT WHEN VI = 1.05V	3
FIGURE 5 CE AMPLIFIER 8 VOLTS, CIRCUIT	3
FIGURE 6 CE AMPLIFIER VB AND VO	4
FIGURE 7 CE AMPLIFIER VOUT AND VB USING RMS	4
FIGURE 8 CE AMPLIFIER WITH VOLTAGE DIVIDER CIRCUIT AFTER SHORTING THE 100 KΩ RESISTOR CIRCUIT	5
FIGURE 9 CE AMPLIFIER WITH VOLTAGE DIVIDER CIRCUIT AFTER SHORTING THE 100 KΩ RESISTOR SIMULATION	5
FIGURE 10 CE AMPLIFIER WITH VOLTAGE DIVIDER CIRCUIT AFTER REPLACE THE 100 KΩ RESISTOR WITH 47KΩ SIMULATION	6
FIGURE 11 COMMON COLLECTOR TRANSISTOR AMPLIFIER CIRCUIT AND SIMULATION	7
FIGURE 12 COMMON COLLECTOR TRANSISTOR AMPLIFIER VO, P-P ≈ 2V	7
FIGURE 13 COMMON COLLECTOR TRANSISTOR AMPLIFIER II AND IOUT	8
FIGURE 14 COMMON COLLECTOR TRANSISTOR AMPLIFIER ZOUT CIRCUIT	8
FIGURE 15 COMMON COLLECTOR TRANSISTOR AMPLIFIER V, ZOUT	9
FIGURE 16 COMMON COLLECTOR TRANSISTOR AMPLIFIER I, ZOUT	9
FIGURE 17 COMMON COLLECTOR TRANSISTOR AMPLIFIER VRMS FOR R2	10
FIGURE 18 COMMON BASE AMPLIFIER CIRCUIT	11
FIGURE 19 COMMON BASE AMPLIFIER CIRCUIT SIMULATION	11
FIGURE 20 COMMON BASE AMPLIFIER VOUT, P-P = 2V	12
FIGURE 21 COMMON BASE AMPLIFIER II AND IOUT	12
FIGURE 22 COMMON BASE AMPLIFIER V(RMS) FOR 0.47K RESISTOR	13
FIGURE 23 COMMON BASE AMPLIFIER WITH 10K RESISTOR	13
FIGURE 24 COMMON BASE AMPLIFIER WITH 10K RESISTOR VRMS SIMULATION	13
FIGURE 25 COMMON BASE AMPLIFIER ZOUT	14
FIGURE 26 COMMON BASE AMPLIFIER VRMS FOR ZOUT	14
FIGURE 27 COMMON BASE AMPLIFIER IRMS FOR ZOUT	14

Table of Tables

TABLE 1 CE VOLTAGE AND CURRENT VALUES	3
TABLE 2 CC VOLTAGE AND CURRENT VALUES	7
TABLE 3 COMMON COLLECTOR TRANSISTOR AMPLIFIER RESULTED VALUES.....	10
TABLE 4 COMMON BASE AMPLIFIER VALUES.....	11
TABLE 5 COMMON BASE AMPLIFIER RESULTS.....	15

Prelab instructions:

1. Simulate the circuits in the procedure section and determine the required values (set the parameters that must be assigned by the instructor in the procedure to proper values).
2. Verify if Simulation Results match the expected results

Procedure and Discussion

Part 1: Common emitter transistor amplifier

1.1: 0 Voltage Ac and Dc (CE amplifier with voltage divider - bias):

First figure shows the CE Amplifier with a Voltage Divider Circuit. The potentiometer (POT) value is set to 10 kHz. The sinusoidal source frequency is set to 1 kHz while the amplitude is set to zero, since v0 connected to nothing as an open circuit, R8 with value 100MEGA has been used as replacement.

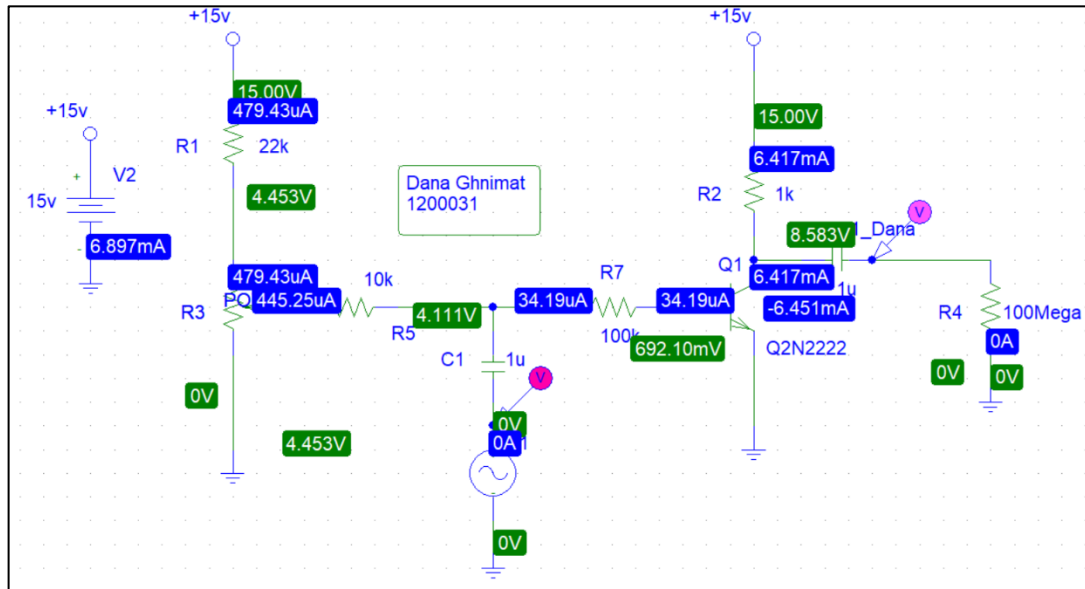


Figure 1 CE amplifier with 0 volt.

1.2: 8 Voltage DC value:

After the base bias potentiometer had been adjusted to 11.05k Ω for a DC collector voltage (VC) for 8 volts.

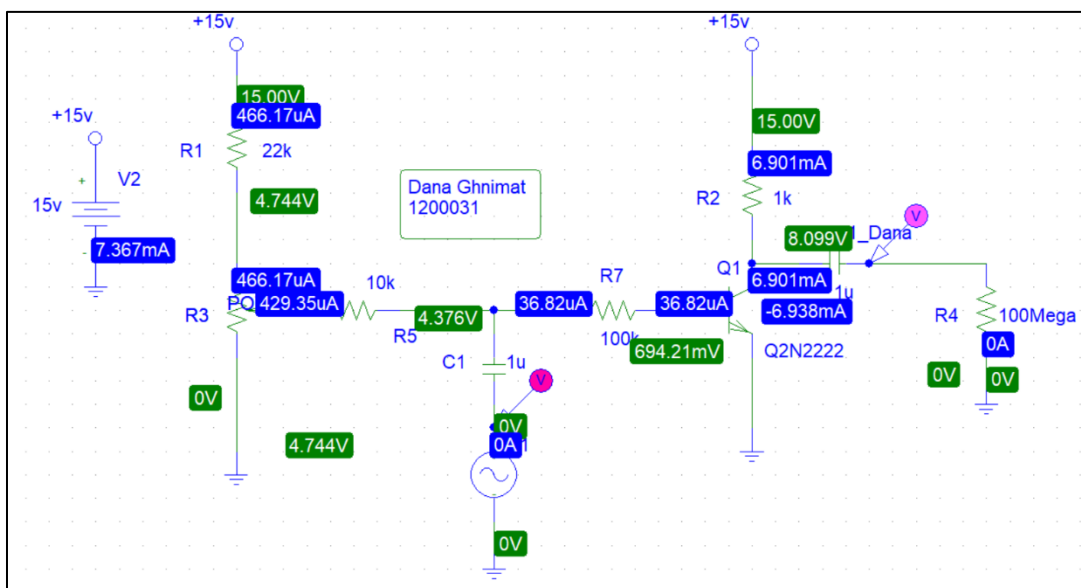


Figure 2 CE amplifier with DC power supply

Table 1 CE Voltage and Current values

IC	IB	VCE	VBE	VBC
6.901mA	36.82μA	8.099V	694.21mV	7.4047V

1.3: When voltage 1V AC:

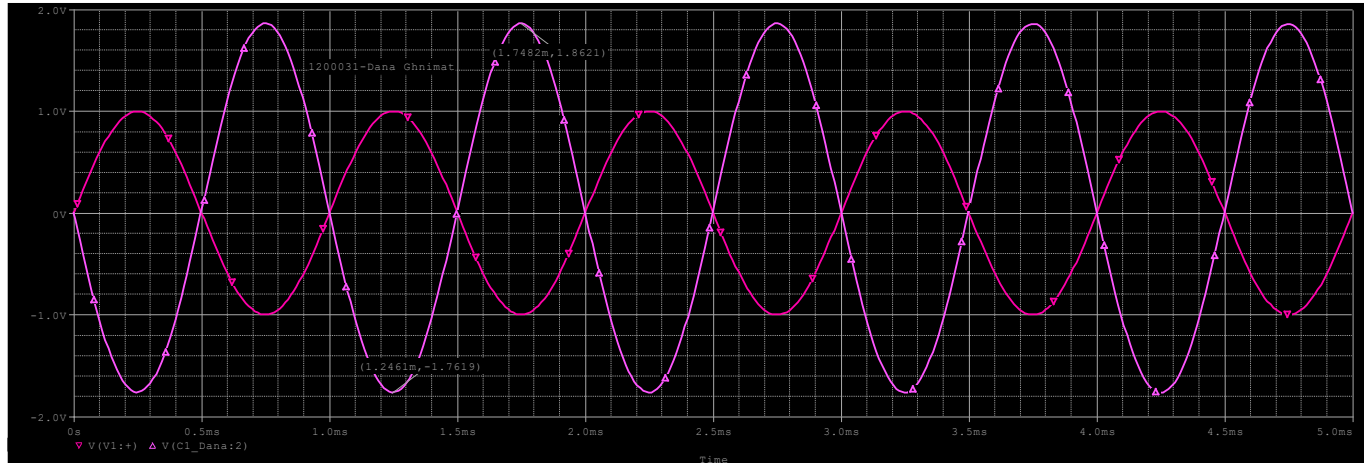


Figure 3 CE Amplifier Vout when $V_i = 1V$

1.4: 8 Voltage DC value and 2.2volt AC:

To get to value of V_0 to around 8Vp-p, The Voltage input has been tested to mode around the double of input until it appear into 2.2Volt (4.4 Vp-p).

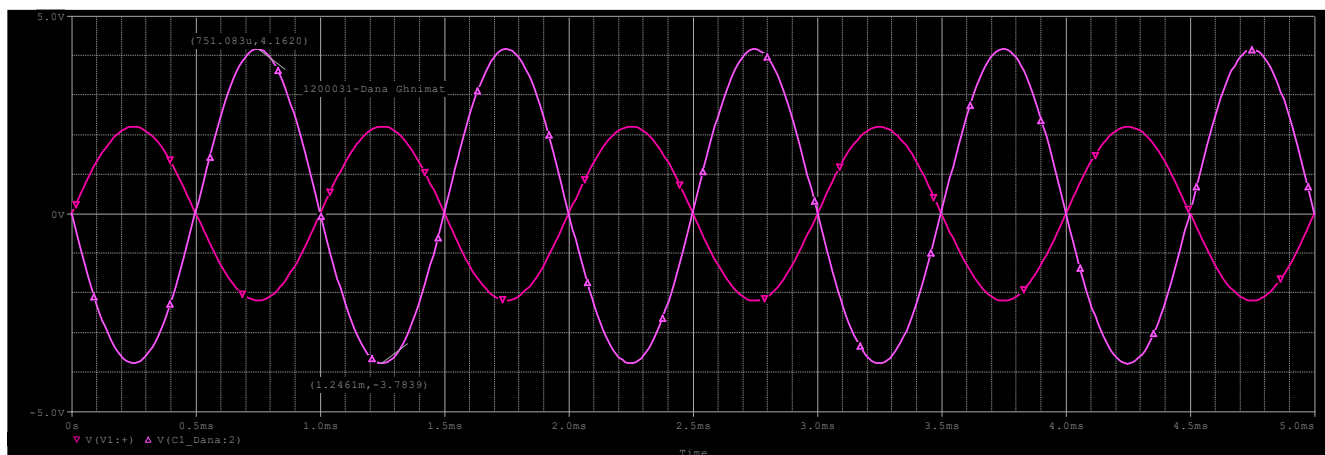


Figure 4 CE amplifier Vout when $V_i = 1.05V$

Circuit and parameters:

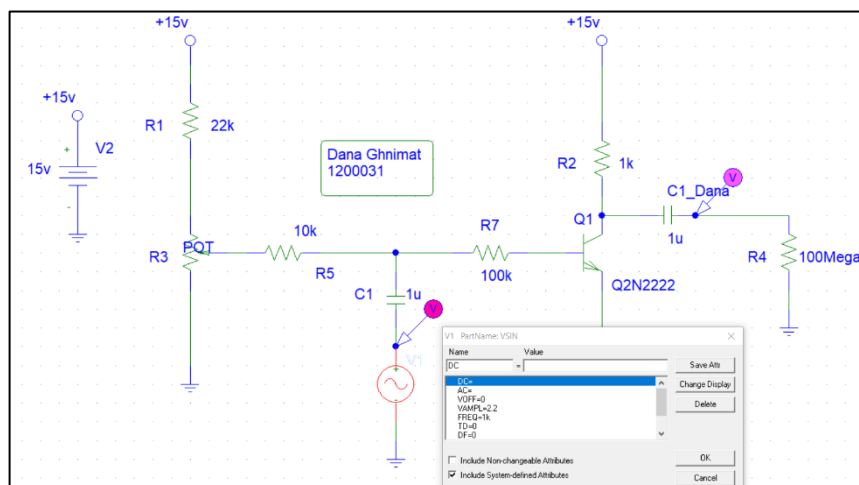


Figure 5 CE amplifier 8 Volts, circuit

$$V_{O_{p-p}} = 7.9459 \text{ V}, V_{in_{p-p}} = 4.4 \text{ V}$$

$$\begin{aligned} A_v &= \frac{V_o}{V_{in}} \\ &= 7.9459 / 4.4 \text{ V} \\ &= 1.8058 \end{aligned}$$

1.5: Gain calculation on Vb and Vo.

First, the oscilloscope connected on Vb.

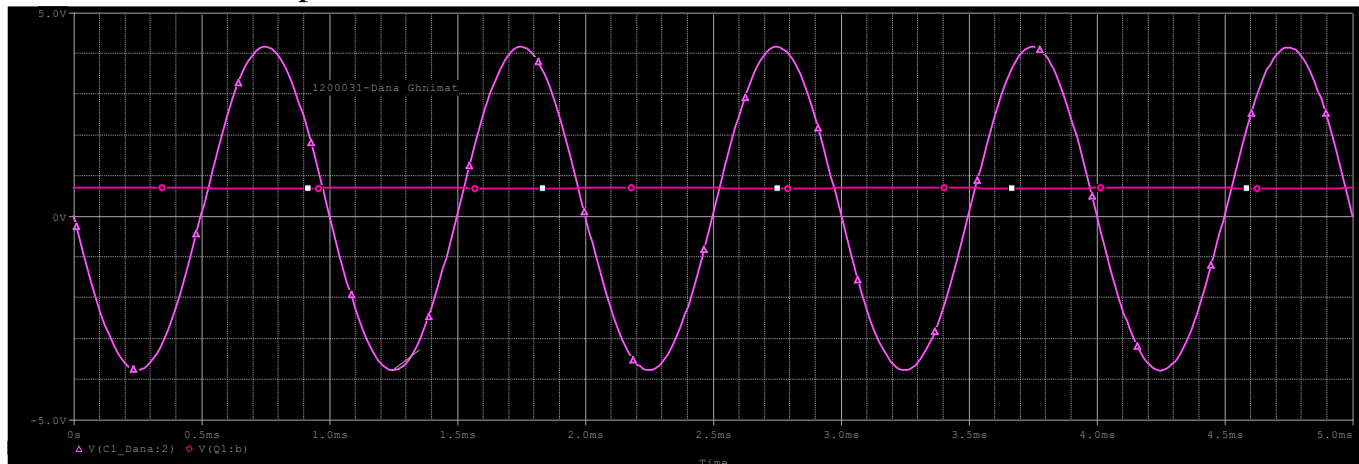


Figure 6 CE amplifier Vb and Vo

Since the values in Figure 6 not cleared, The RMS value is used as shown in Figure 7,

$$V_{O_{rms}} = 2.8126 \text{ V}, V_{in_{rms}} = 691.581 \text{ mV}$$

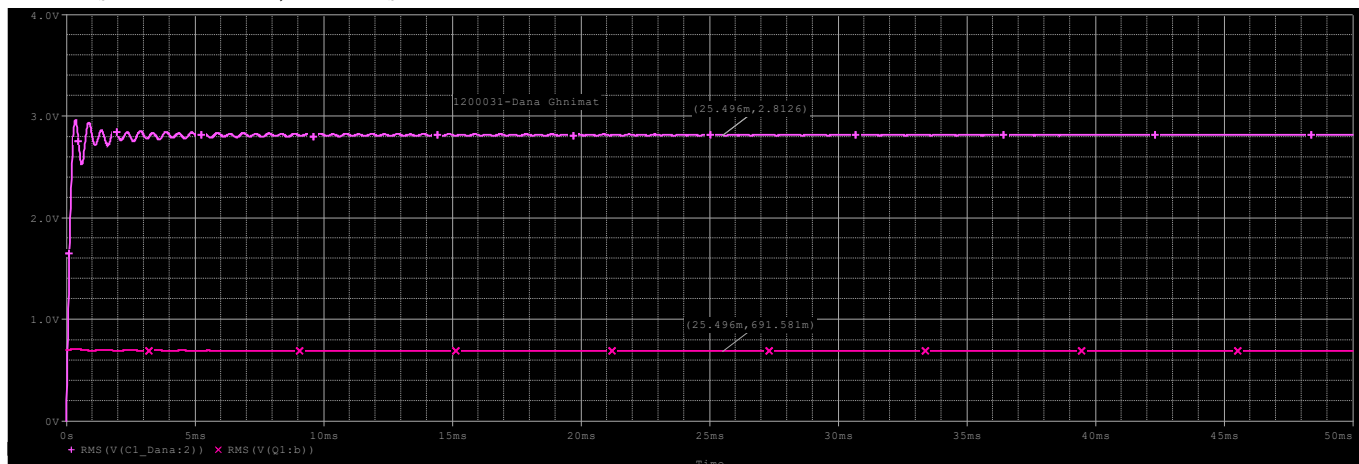


Figure 7 CE Amplifier Vout and VB using RMS

$$\begin{aligned} A_v &= \frac{V_{O_{rms}}}{V_{in_{rms}}} \\ &= 2.8126 / 0.6915 \\ &= 4.06691 \end{aligned}$$

1.6: The effect of the 100 kΩ Resistor

After removing 100k resistor:

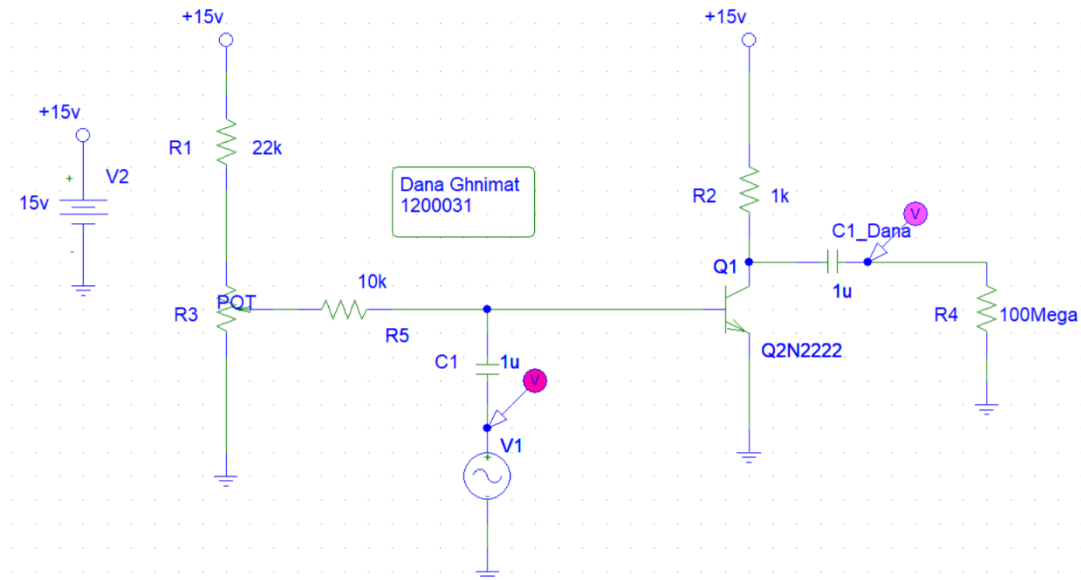


Figure 8 CE Amplifier with Voltage Divider Circuit after shorting the 100 kΩ Resistor Circuit

Simulation:

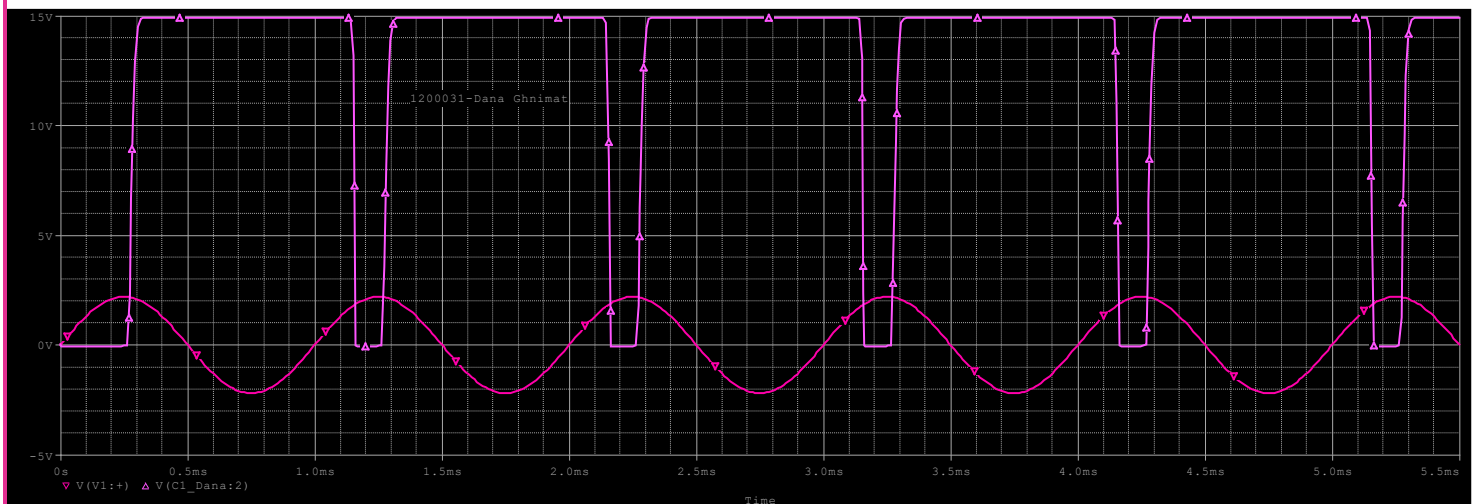


Figure 9 CE Amplifier with Voltage Divider Circuit after shorting the 100 kΩ Resistor Simulation

As shown in Circuit simulation $V_o = 15V$ when $V_{in} = 4.4V$.

$$\begin{aligned} A_v &= \frac{V_o}{V_{in}} \\ &= 15 / 4.4 \\ &= 3.4090 \end{aligned}$$

The 100 kΩ Resistor have high effect of the voltage gain, which equals to:

$$A_{V_{R100k \text{ effect}}} = A_{V, \text{old}} - A_{V, \text{new}} = 4.06691 - 3.4090 = 0.65791.$$

When replace 100k with 47k Ω

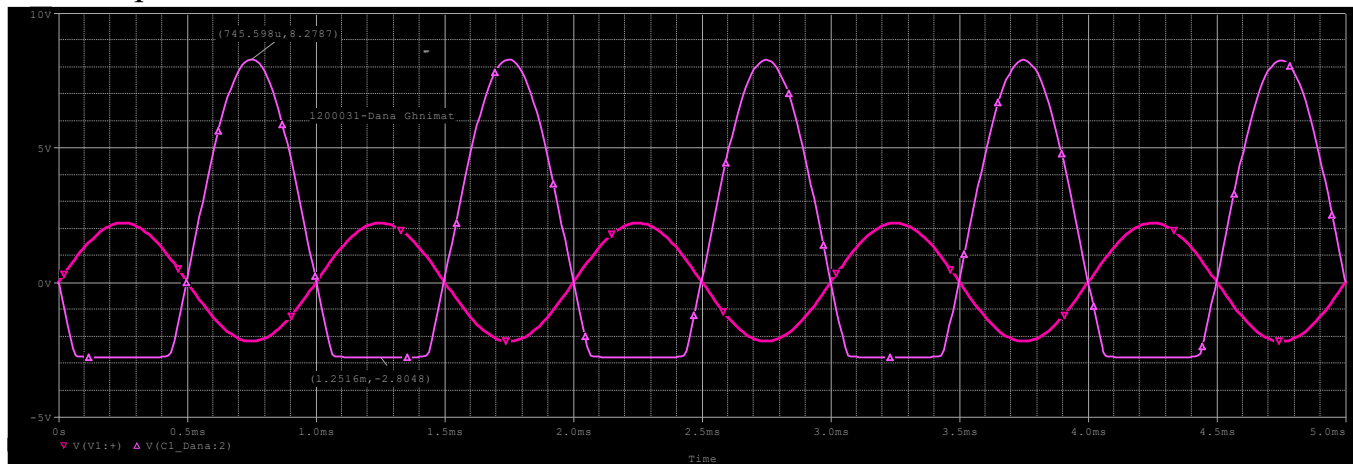


Figure 10 CE Amplifier with Voltage Divider Circuit after replace the 100 k Ω Resistor with 47k Ω Simulation

As shown in Circuit simulation $V_{O_{p-p}} = 11.0835V$ when $V_{in_{p-p}} = 4.4V$.

$$\begin{aligned} A_v &= \frac{V_o}{V_{in}} \\ &= 11.0835 / 4.4 \\ &= 2.5189 \end{aligned}$$

The 100 k Ω Resistor have high effect of the voltage gain, which equals to:

$$A_{v_{R47k \text{ effect}}} = A_{v, \text{old}} - A_{v, \text{new}} = 4.06691 - 2.5189 = 1.54801$$

2.3: Calculating Ai and Zi:

To measure Ai and Zi I on the input and I on R2 resistor:

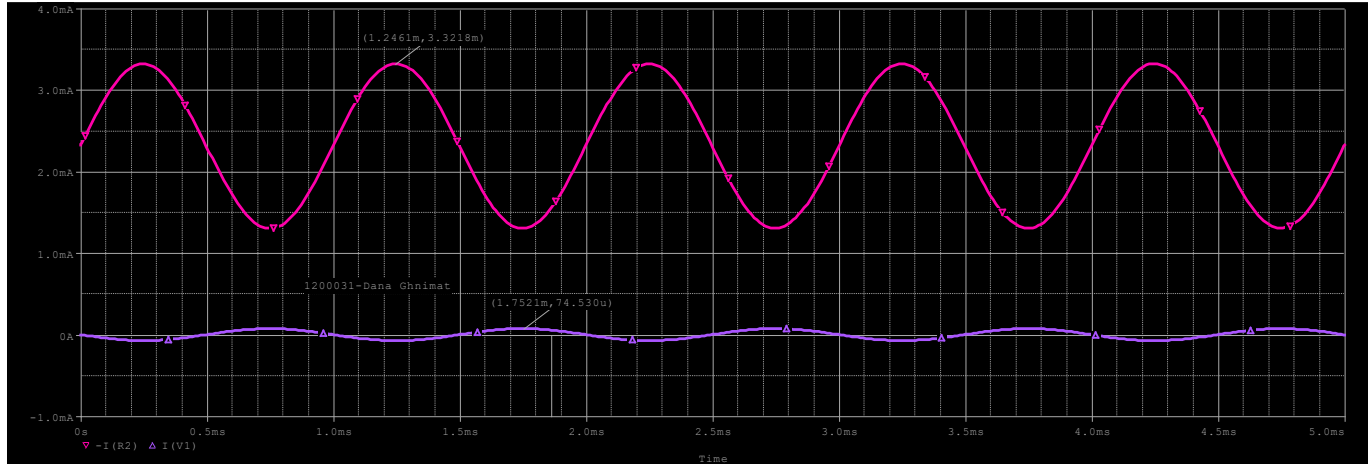


Figure 13 Common Collector Transistor Amplifier Ii and Iout

As the figure 13 shows that $I_{o, \text{peak}} = 3.3218\text{mA}$, while $I_{in, \text{peak}} = 74.530\mu\text{A}$

$$\begin{aligned} A_i &= \frac{I_o}{I_{in}} \\ &= 3.3218 / 74.530\mu \\ &= 44.5699 \end{aligned}$$

Since $V_{in} = 8.39\text{V}$, and $I_{in} = 74.530\mu\text{A}$. Then

$$\begin{aligned} Z_i &= \frac{V_{in}}{I_{in}} \\ &= 8.39 / 74.530\mu \\ &= 112.57\text{k}\Omega \end{aligned}$$

2.4: Calculating Zout:

As shown in figure 14, to measure Zout, a generator on the output is connected and removed the original sine wave generator is replaced with short circuit.

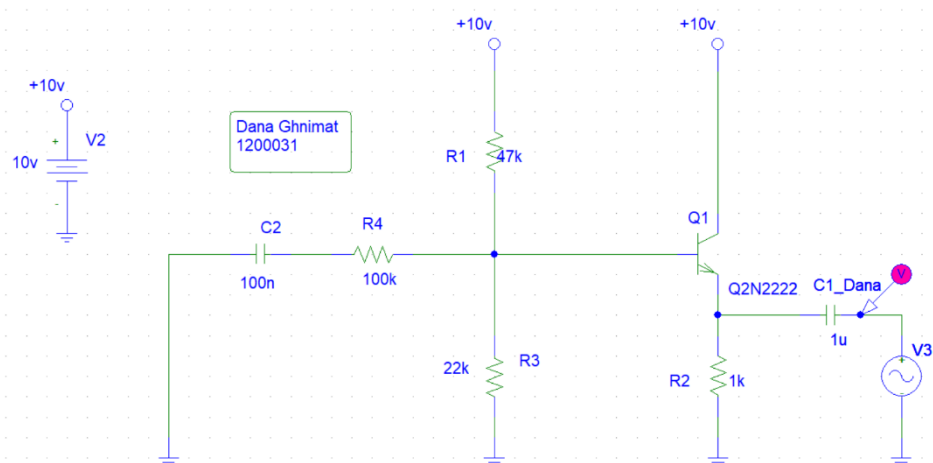


Figure 14 Common Collector Transistor Amplifier Zout circuit

in the simulation to find mean value to find V_{rms} , Z_{out} : which is 5.9413V

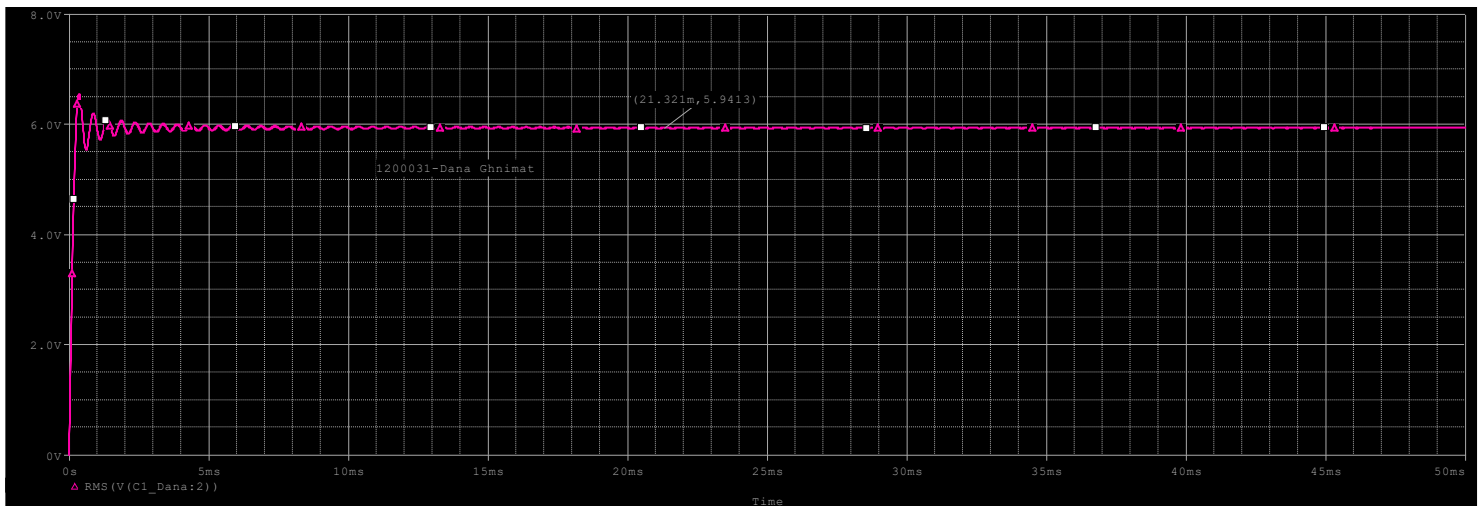


Figure 15 Common Collector Transistor Amplifier V, Z_{out}

Simulation for I_{rms} , Z_{out} which is 16.485mA.

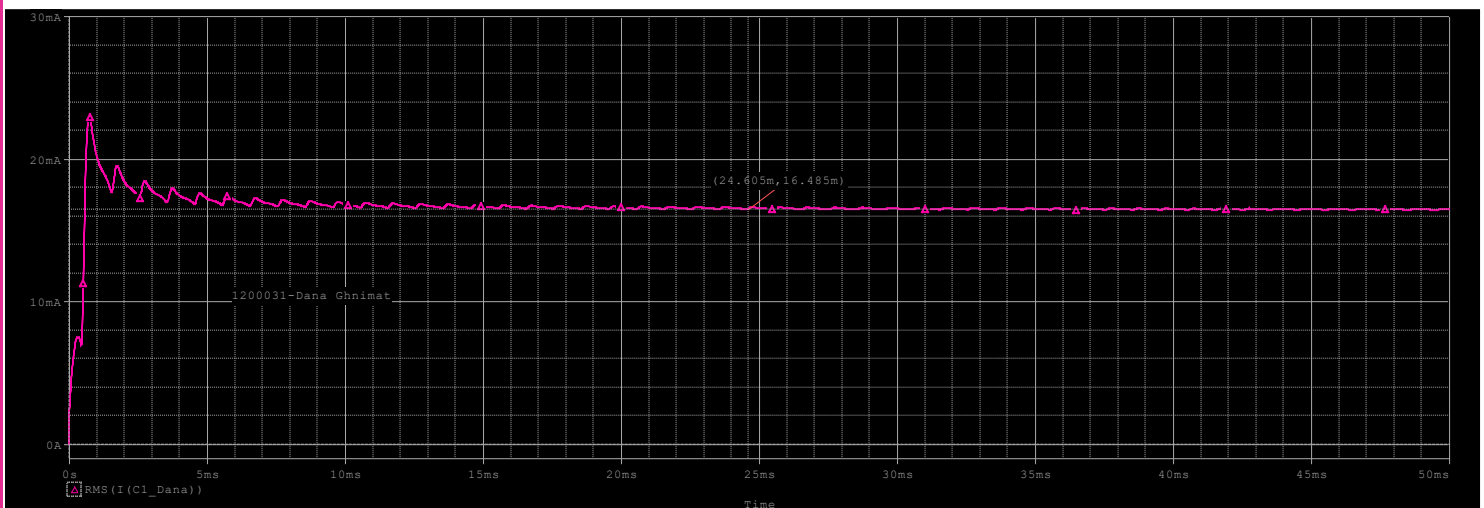


Figure 16 Common Collector Transistor Amplifier I, Z_{out}

$$\begin{aligned}
 Z_{out} &= \frac{V_o}{I_o} \\
 &= 5.9413 / 16.485\text{m} \\
 &= 36.0406
 \end{aligned}$$

2.5: I_{in} for 100k Ω Register:

V_{rms} is used for R2, $V_{100k, rms} = 3.0749$

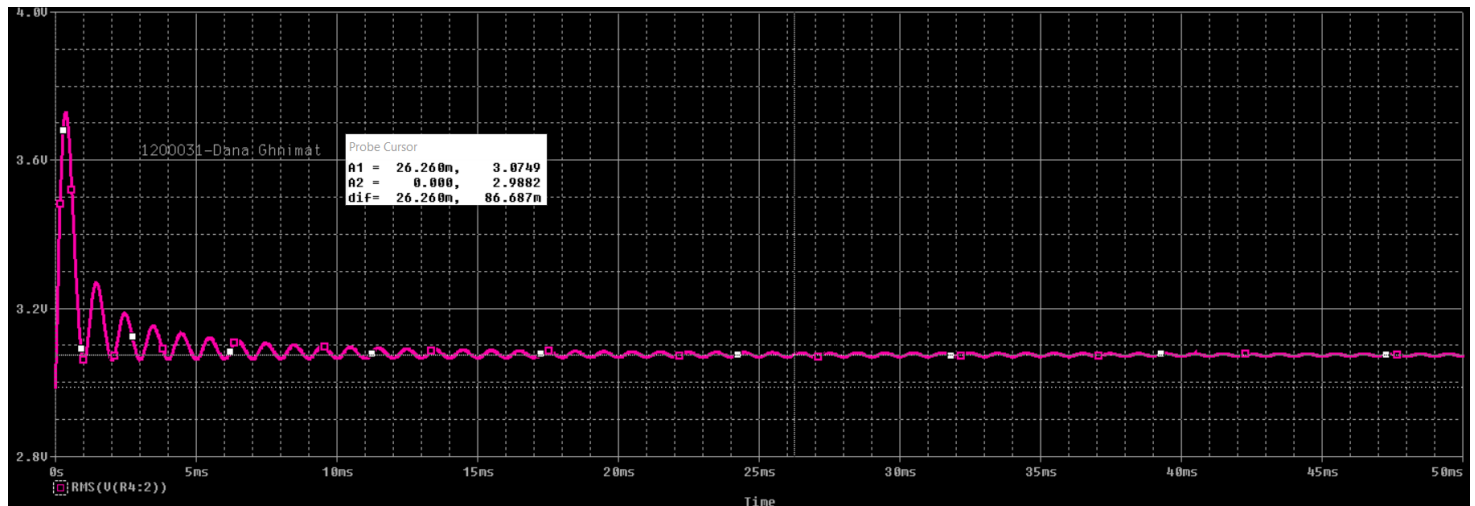


Figure 17 Common Collector Transistor Amplifier V_{rms} for R2

$$\begin{aligned}
 I_{100K,R} &= \frac{V_{rms}}{R} \\
 &= 3.0749 / 100k \\
 &= 3.0749 * 10^{-5} \text{ A} \\
 &= 30.749 \mu\text{A}
 \end{aligned}$$

Table 3 Common Collector Transistor Amplifier Resulted Values

Quantity	Measured values
V_{in}	8.39V
V_{out}	2V _{P-P}
$V_{100k, RMS}$	3.0749V
I_{out}	16.485mA
Calculated values	
$A_v = V_{out} / V_{in}$	0.1190
$I_{in} = V_{100k, RMS} / 100k$	30.749 μA
$A_i = I_{out} / I_{in}$	44.5699
$Z_{in} = V_{in} / I_{in}$	112.57k Ω
$Z_{out} = V_T / I_T$	36.0406 Ω

A common collector amplifier is used as a buffer. This means the input impedance of this amplifier is very high, while the output impedance is low.

Compared to the common emitter stage, the DC configuration provides less than a unite voltage gain, high input impedance similar to the common emitter stage, low output impedance, and an in-phase relationship between the input and output signals.

The Emitter followers are typically used when high input impedance and low output impedance are required, so they are used for matching impedances.

Part3: Common base transistor amplifier:

3.1: Common Base Transistor Circuit:

Common Base amplifier Circuit has been built as in figure 18. As The sinusoidal source frequency sat to 1 kHz and amplitude to zero volt.

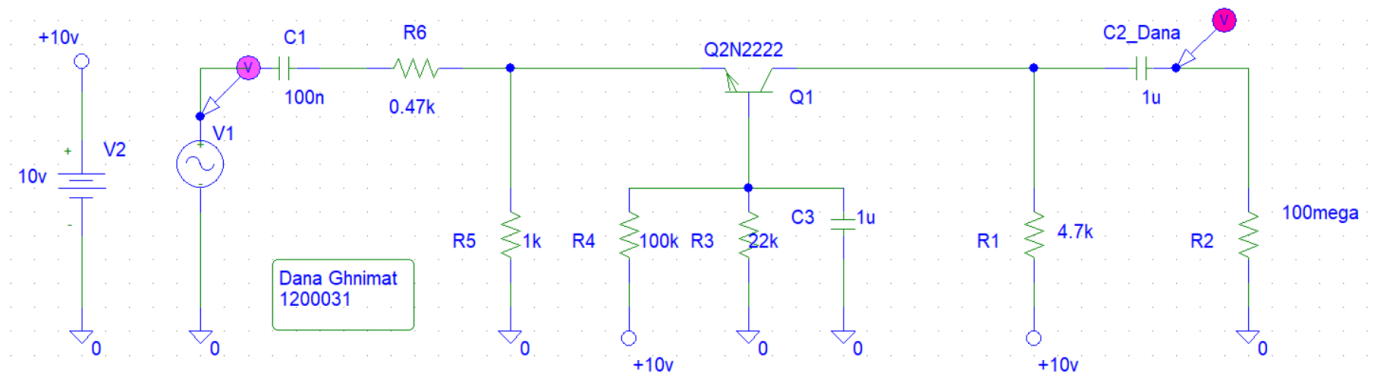


Figure 18 Common Base amplifier Circuit

Simulation:

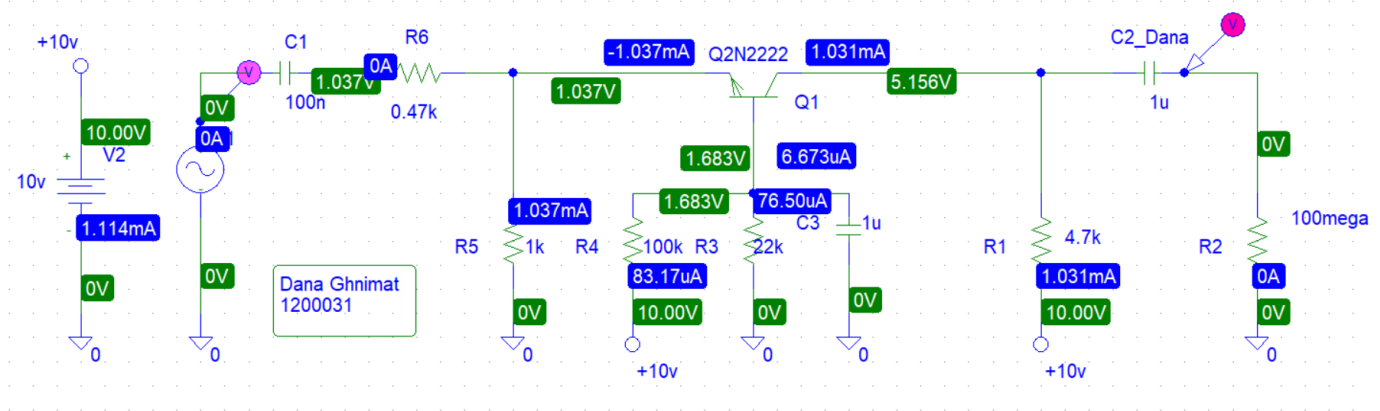


Figure 19 Common Base amplifier Circuit simulation

Table 4 Common Base amplifier values

IC	IB	VC	VB	VE
1.037mA	6.673μA	1.037V	1.683V	5.156V

$$V_{BE} = V_B - V_E = 1.683 - 1.037 = 0.646V$$

$$V_{BC} = V_B - V_C = 1.683 - 5.156 = -3.473V$$

$$V_{CE} = V_C - V_E = 5.156 - 1.037 = 4.119V$$

3.2: Setting $V_{out, p-p}$ to 2V:

To get $V_{out, p-p} \approx 2V$. i.e. $V_{out, peak} \approx 1V$. is by V_{in} is sat to 0.37v as shown below:

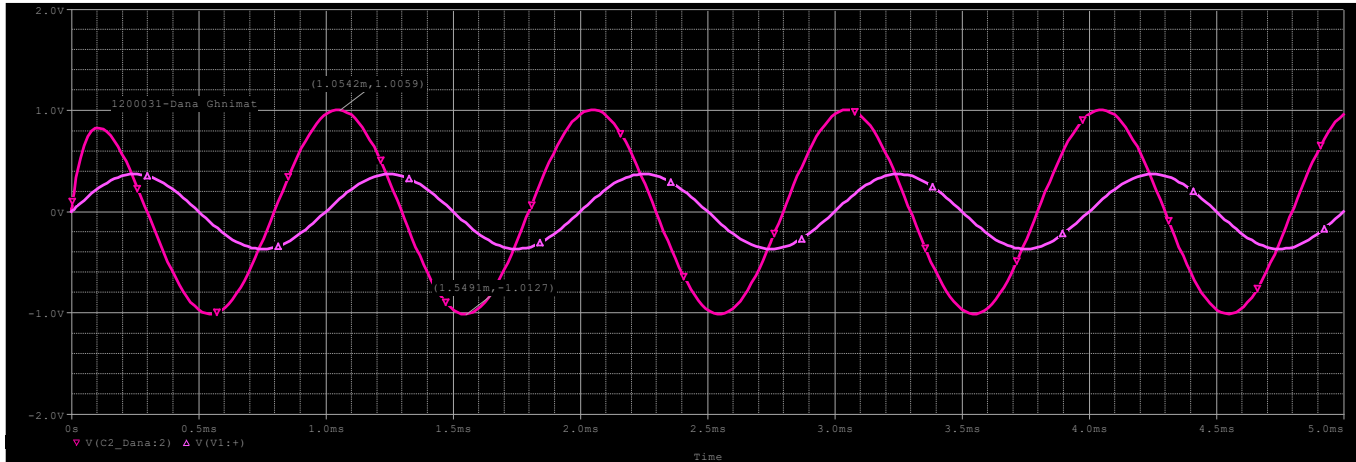


Figure 20 Common Base amplifier $V_{out, p-p} = 2V$

$$\begin{aligned} A_v &= \frac{V_o}{V_{in}} \\ &= 1.0059 / 0.37 \\ &= 2.7186 \end{aligned}$$

3.3: Calculating Z_i and A_i :

To measure A_i , we get $I_{i, peak} = 230.814\mu A$ and $I_{out, peak} = 1.2547mA$ as shown in figure 21

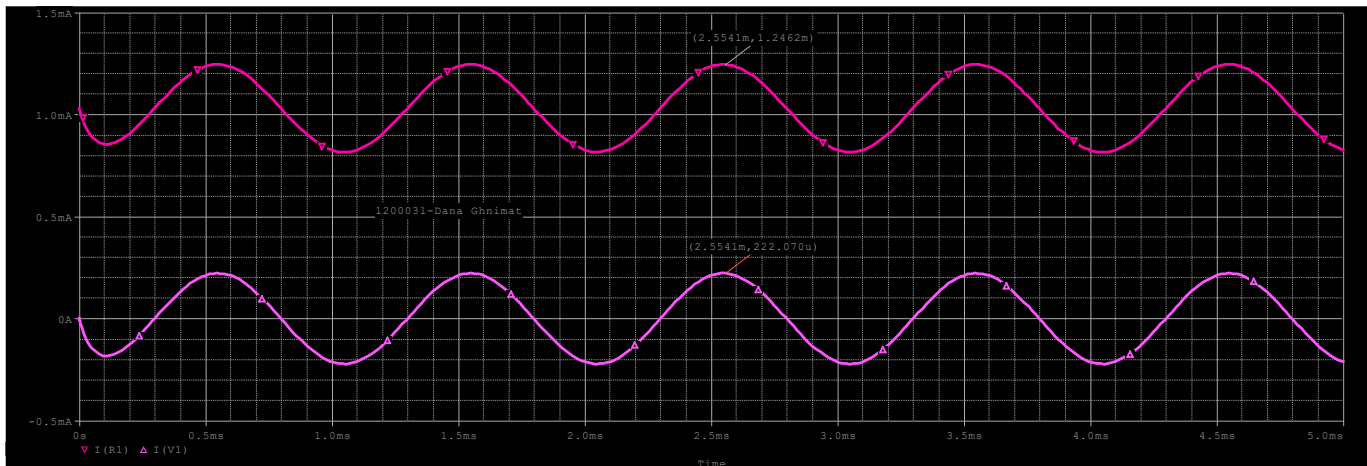


Figure 21 Common Base amplifier I_i and I_{out}

$$\begin{aligned} A_i &= \frac{I_o}{I_{in}} \\ &= 1.2462m / 222.070\mu \\ &= 5.6117 \end{aligned}$$

Since $V_{in} = 0.37V$, and, $I_{i, peak} = 222.070 \mu A$, Then

$$\begin{aligned} Z_i &= \frac{V_{in}}{I_{in}} \\ &= 0.37 / 222.070 \mu \\ &= 1.66614k\Omega \end{aligned}$$

3.4: V across 0.47kΩ Resistor:

To value the Voltage across R= 0.47kΩ, RMS values has been taken.

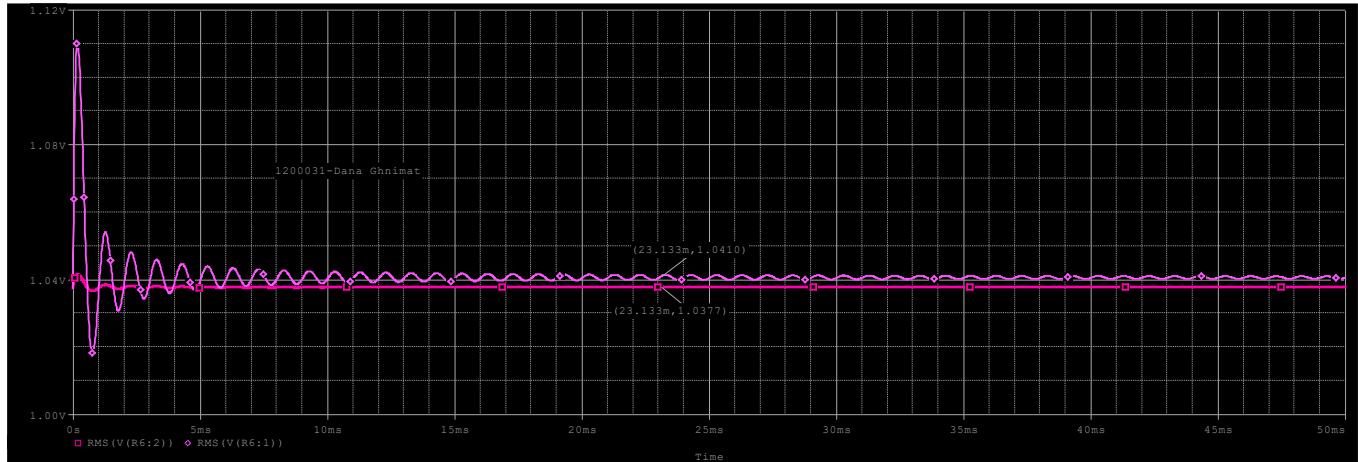


Figure 22 Common Base amplifier V(rms) for 0.47k resistor

$$V = 1.0410 - 1.0377 = 0.0033V$$

3.5: I_{in} for 10kΩ resistor:

To measure I_{in} for 10k resistor, the 0.47k resistor is replaced with with 10k:

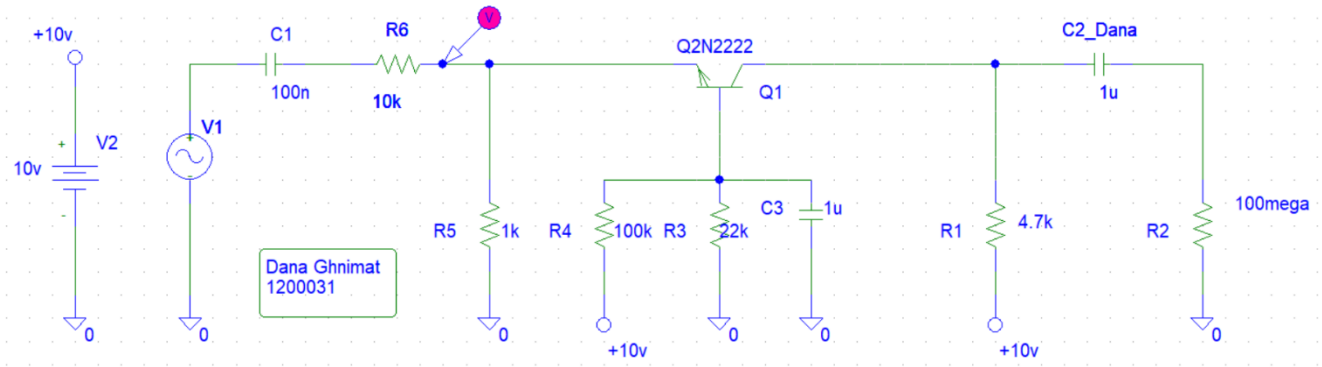


Figure 23 Common Base amplifier with 10k resistor

Simulation using RMS value of V: 1.0374V

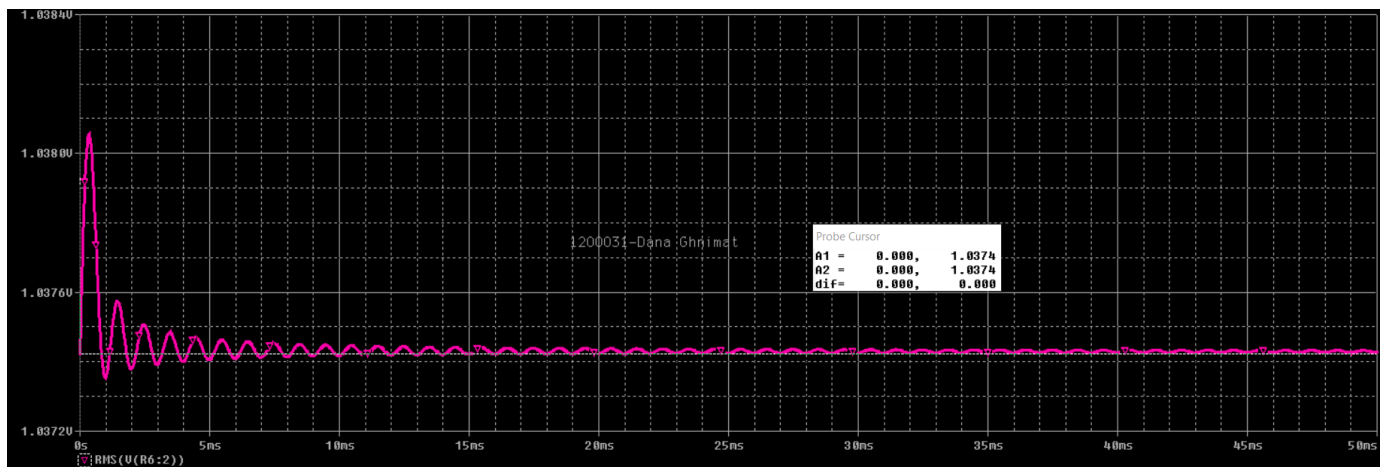


Figure 24 Common Base amplifier with 10k resistor VRMS simulation

$$\begin{aligned} I_{10K, R} &= \frac{V_{rms}}{R} \\ &= 1.0374 / 10k \\ &= 103.74 \mu A \end{aligned}$$

3.6: Calculating Zout:

To measure Zout, the input sine wave generator is replaced with a short circuit, then the generator connected to the output (emitter) via a capacitor, as shown in figure 25.

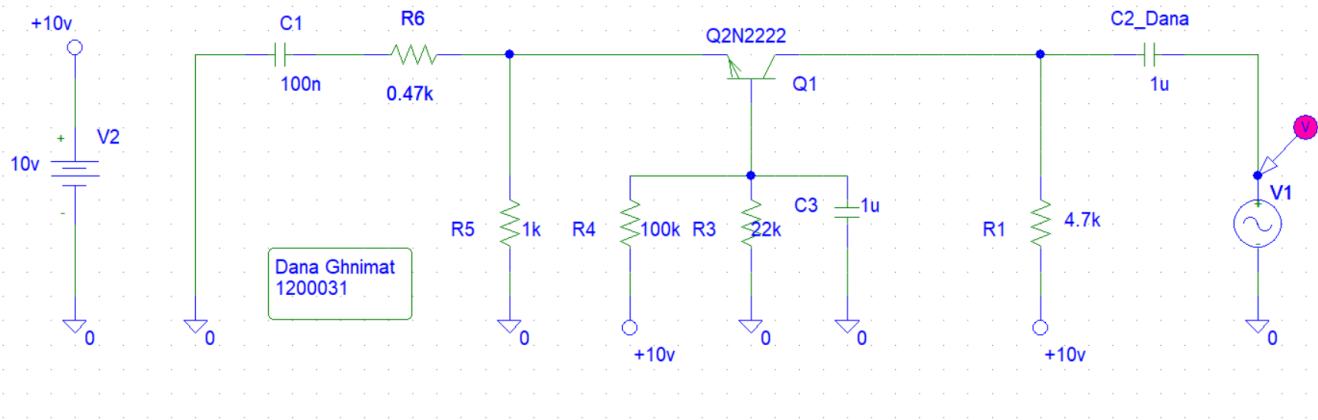


Figure 25 Common Base amplifier Zout

Simulation for Vrms: Vout, rms = 261.625mV.

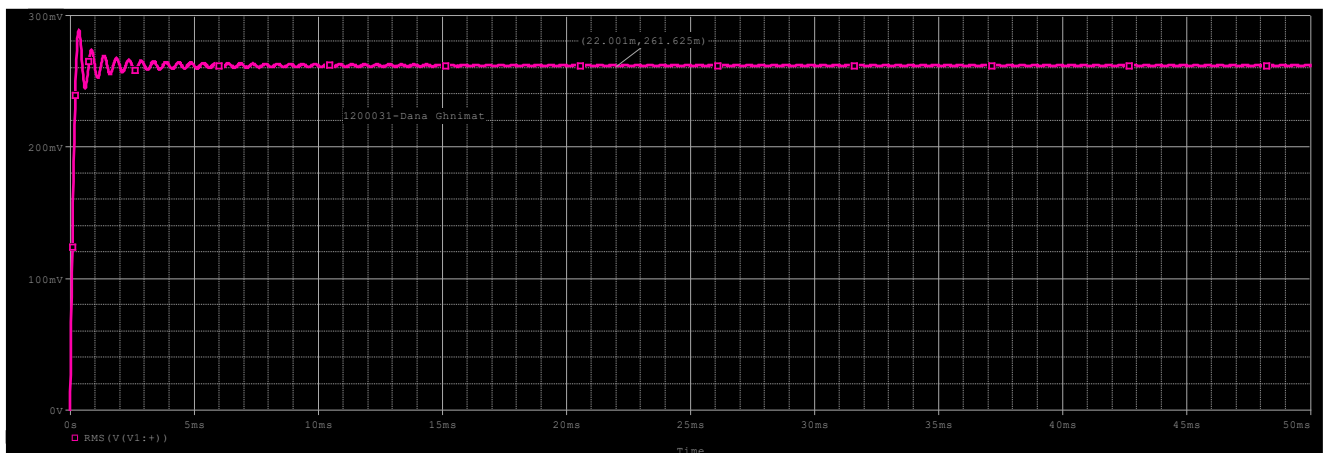


Figure 26 Common Base amplifier Vrms for Zout

Simulation for Irms: Iout, rms = 55.735μA

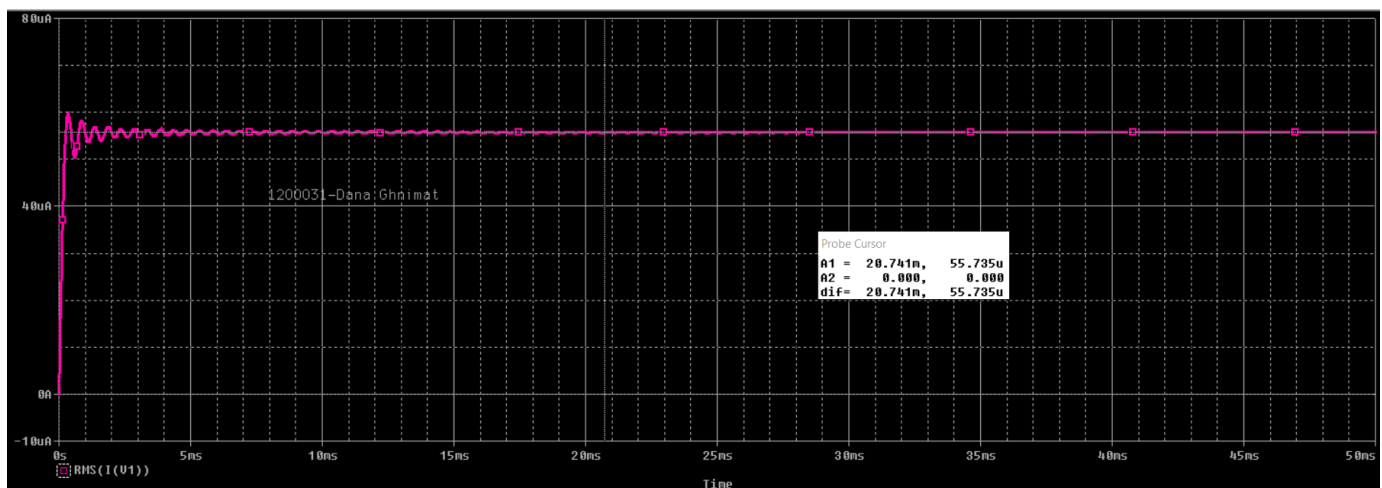


Figure 27 Common Base amplifier Irms for Zout

$$Z_{out} = \frac{V_o}{I_o}$$

$$= 261.625\text{mV} / 55.735\mu\text{A}$$

$$= 4.6941\text{k}\Omega$$

Table 5 Common Base amplifier results

Quantity	Measured values
V_{in}	0.37V
V_{out}	$2V_{P-P}$
$V_{10k, RMS}$	1.0374V
Calculated values	
$A_v = V_{out}/V_{in}$	0.1190
$I_{out} = V_{out} / 4.7k$	0.2127mA
$I_{in} = V_{10k, RMS} / 10k$	103.74 μA
$A_i = I_{out}/I_{in}$	5.6117
$Z_{in} = V_{in} / I_{in}$	1.6661k Ω
$Z_{out} = V_T / I_T$	4.6941k Ω

In a common base (CB) amplifier, the output static voltage, determined by the bias of the transistor, as it is influenced by the input AC signal, due to configuration common basis the output roughly following the input.

Compared to the common emitter amplifier, the CB configuration typically shows lower voltage gain with lower input impedance and lower output impedance.

The common emitter amplifier provides both voltage and current amplification, resulting in higher voltage gain, while the common base stage primarily provides current amplification.